
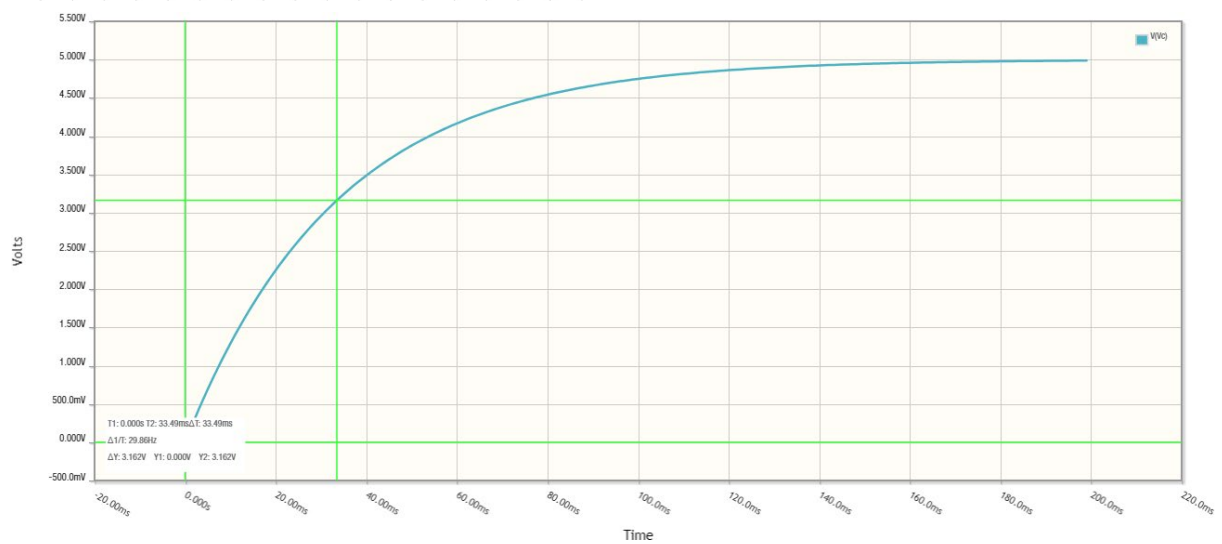


# EEP1 ELogBook – Week 7

AXXXXXXX - Brians Tjipto Meidianto

## Studio

### Activity 1


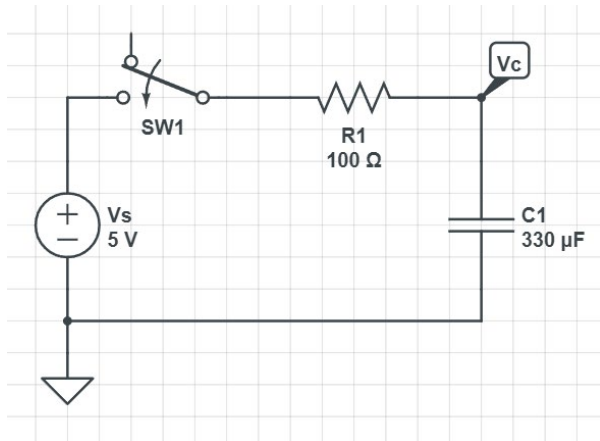


$$T = 33.49\text{ms}$$

$$T = R * C = 100 * (330 * 10^{-6}) = 33\text{ms}$$

Both values are the same.

## Activity 2

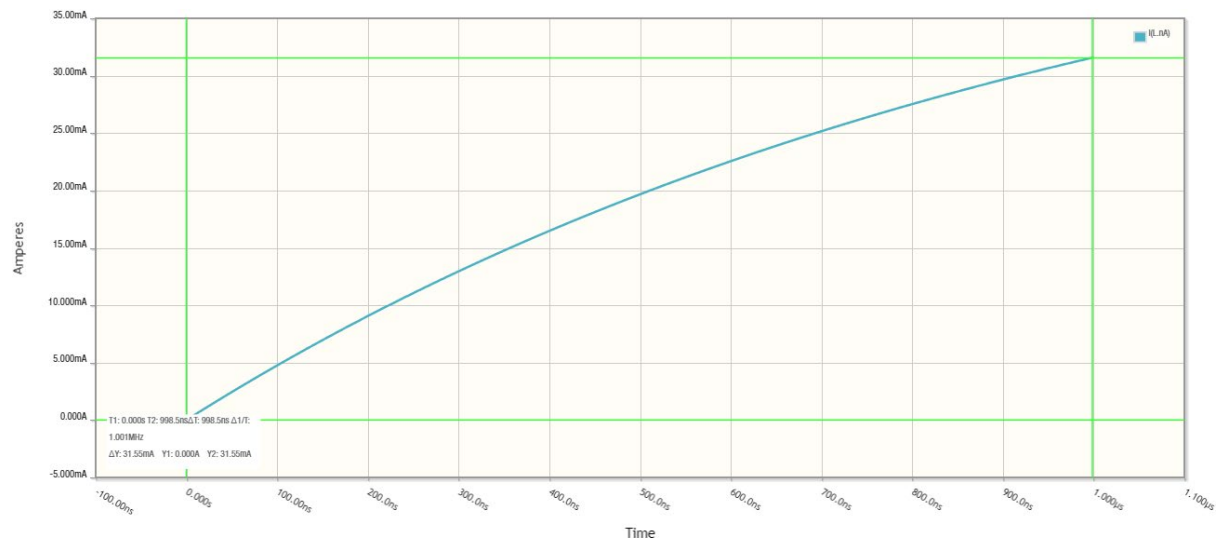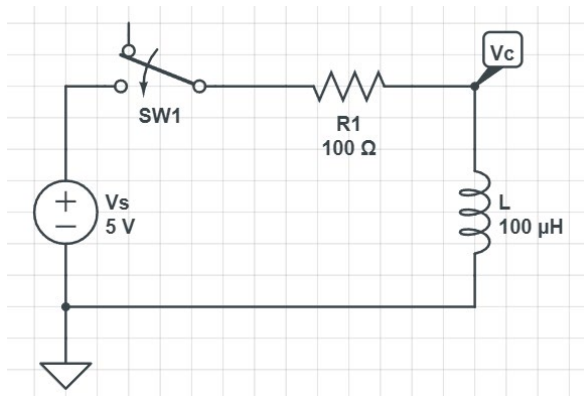


$$T = 998.5\text{ns}$$


$$T = L / R = (100 * 10^{-6}) / 100 = 0.000001 = 1000\text{ns}$$


Roughly the same value

a.  $V_s$  to 10 V, the T decreases

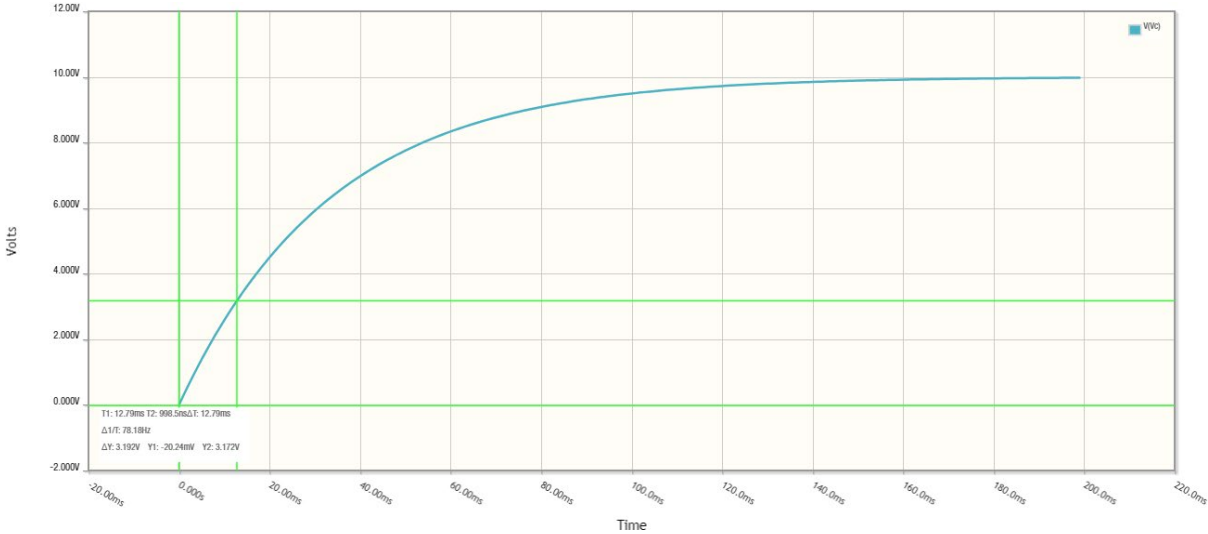


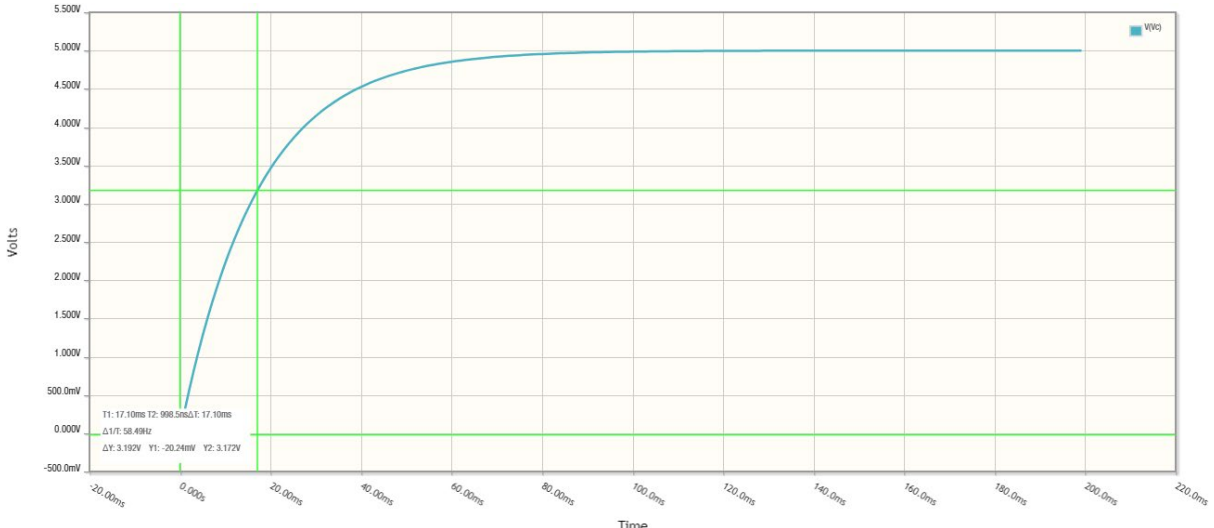b. R to  $50\ \Omega$ , the V / I decrease




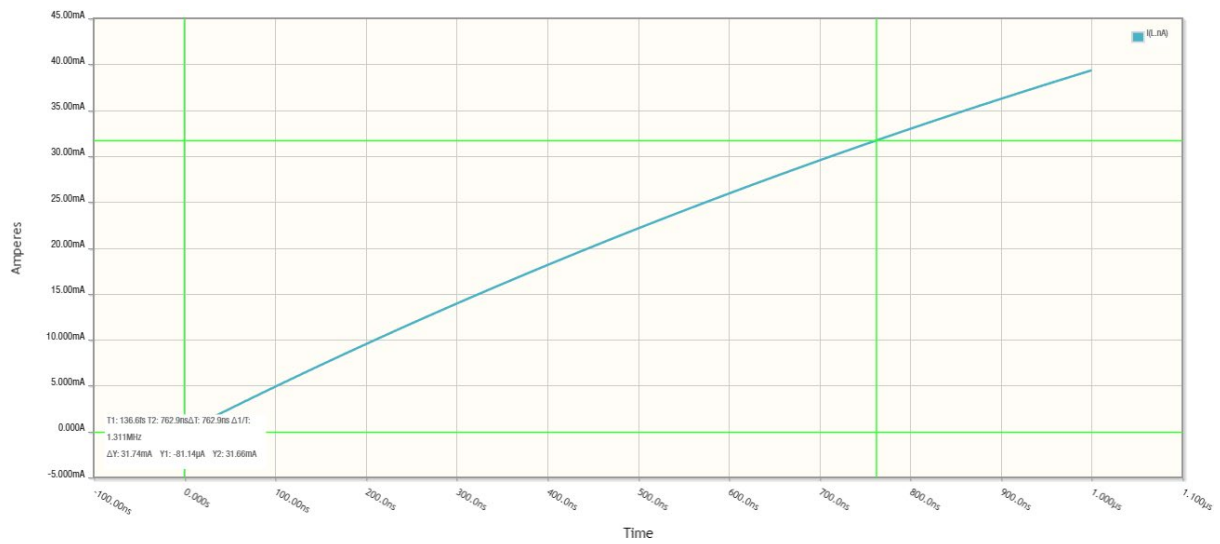

c. C to 660  $\mu$ F, T doubled

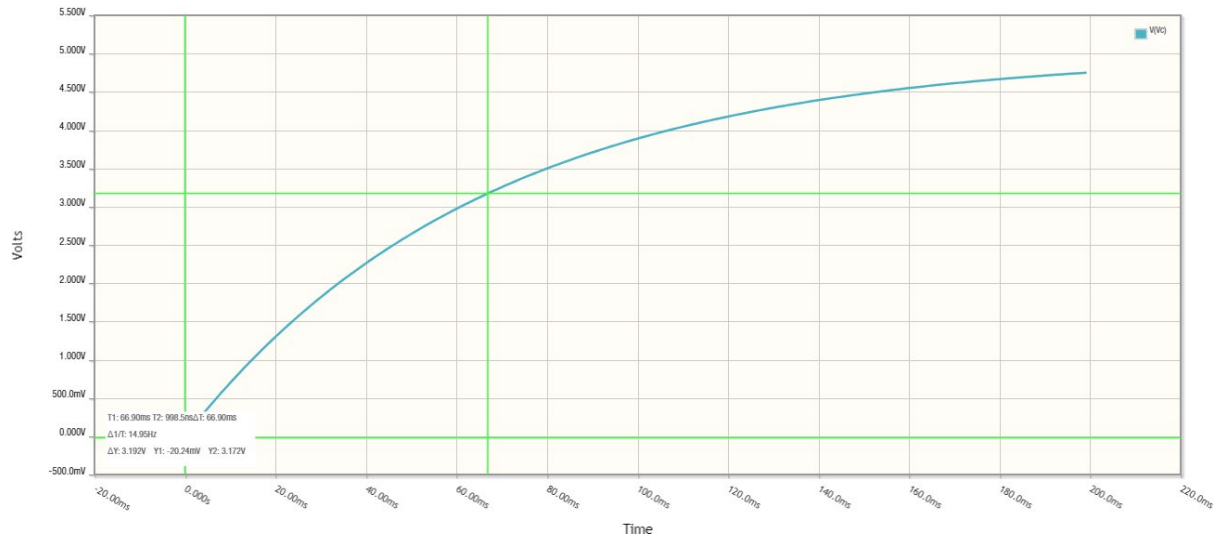

d. L to 200  $\mu$ H, T doubled








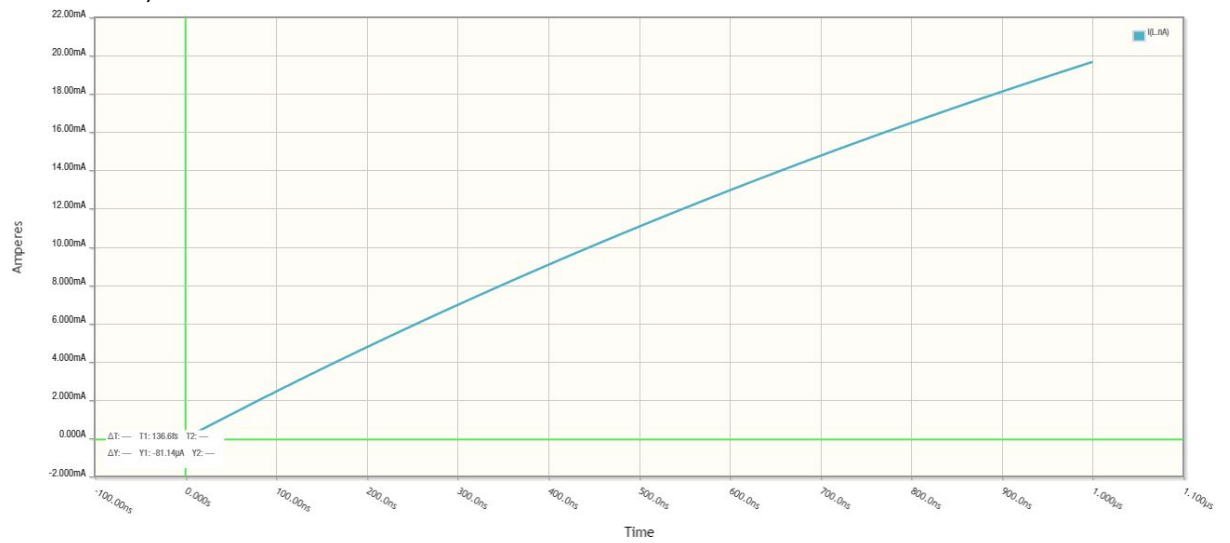


## Lab

### Activity 1



Vs (V)	R ( $\Omega$ )	C ( $\mu$ F)	T (ms)
5	100	330	560
5	100	660	924
5	200	330	584
z10	100	330	308

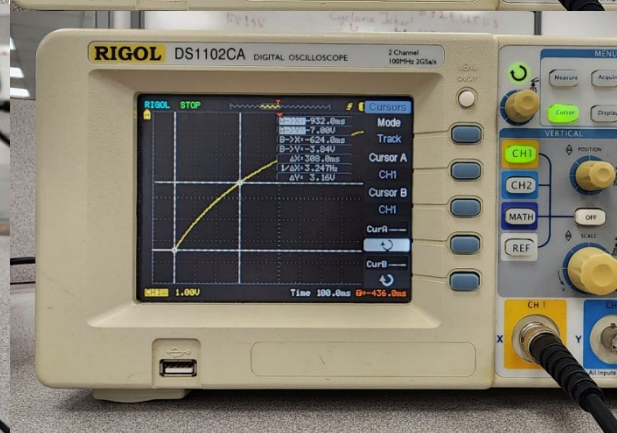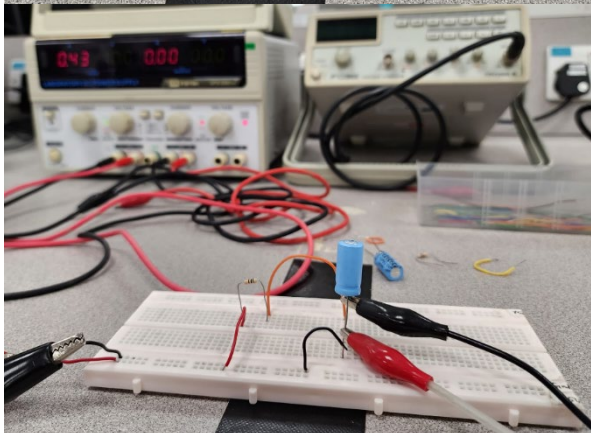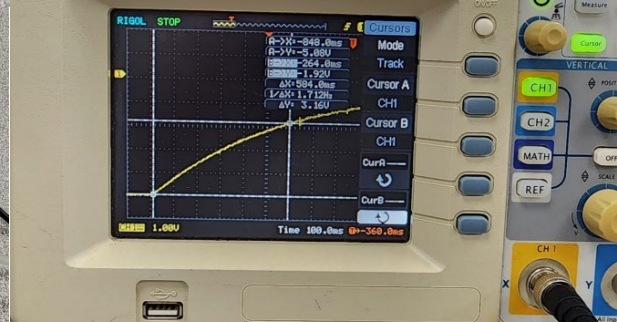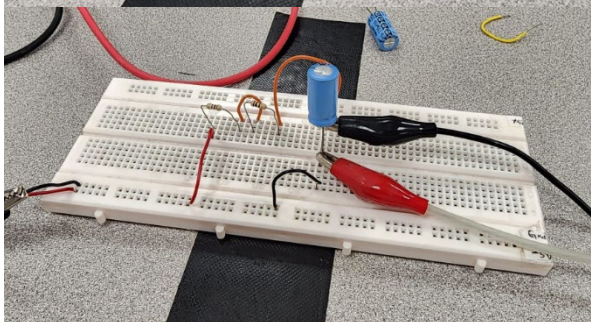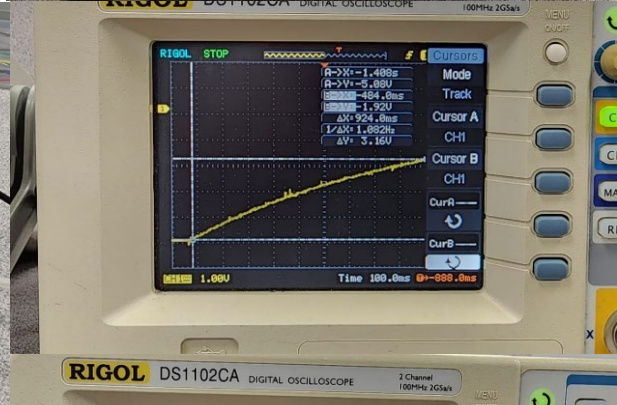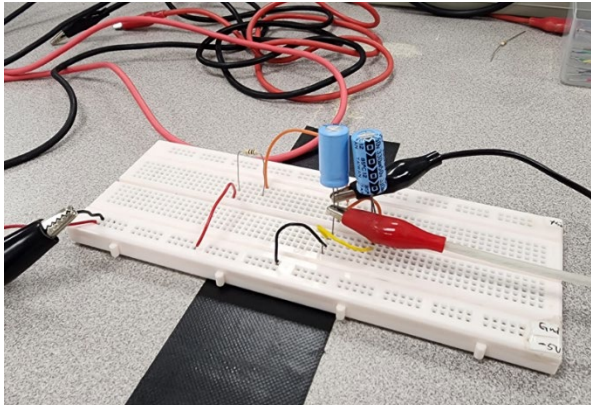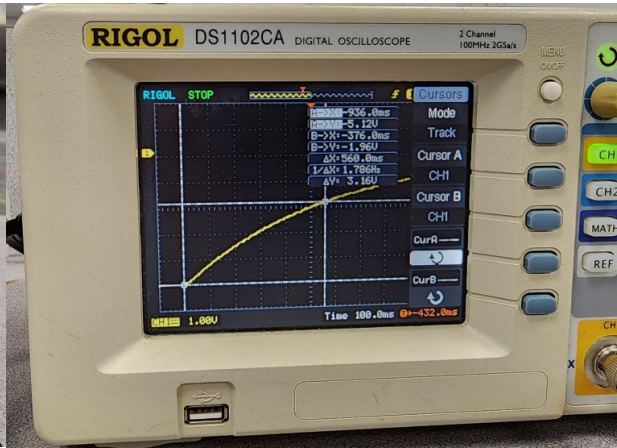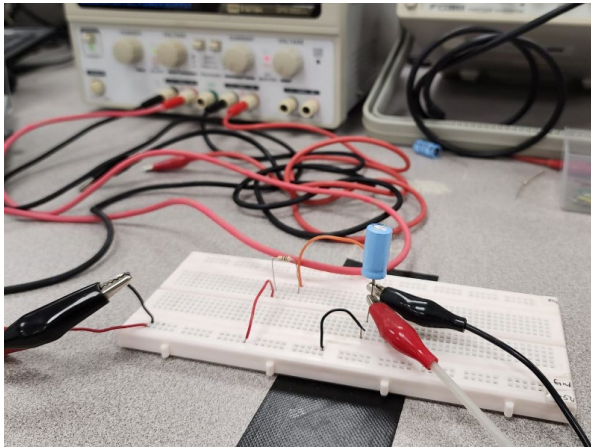When the Capacitance doubled the time constant also doubled, when the Resistance doubled, increased the time constant by a little bit, conversely, the doubling of the Voltage lead to a decrease in the time constant





## Activity 2

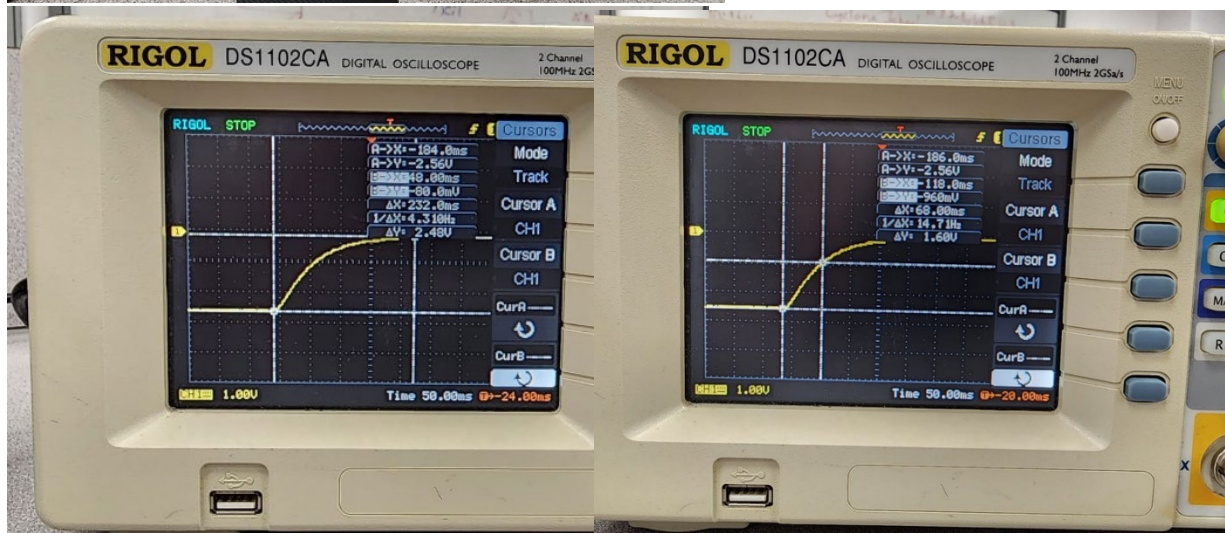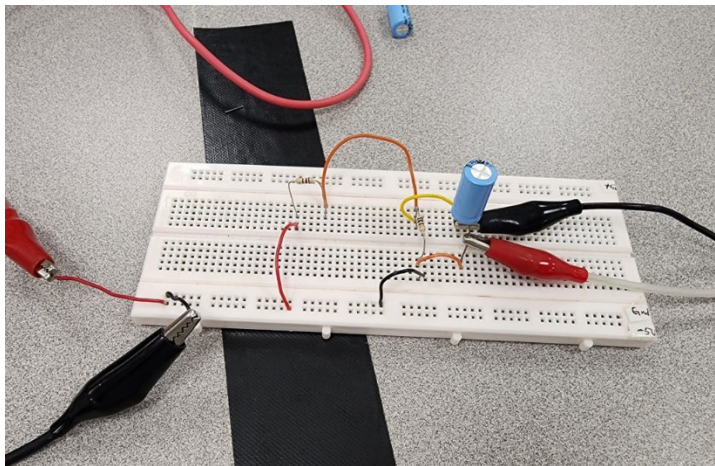

It takes 68ms to get to the time constant

It takes approximately 232ms to get fully discharged at 2.48V


During charging, the capacitor is connected to a voltage source through the resistor.

During discharging, the capacitor discharges through the resistor.

# EEP1 Wk7 - Studio.

## Activity #3

1.

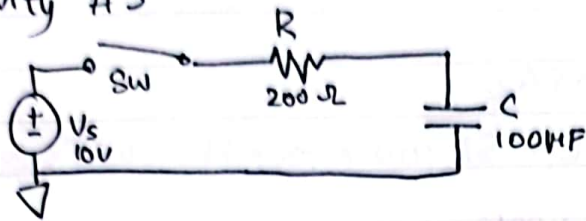


$$a) i(0) = \frac{10}{200} = 0.05 \text{ A}$$


$$b) \tau = RC = 200\Omega \times 100\mu\text{F} = 0.02 \text{ s}$$

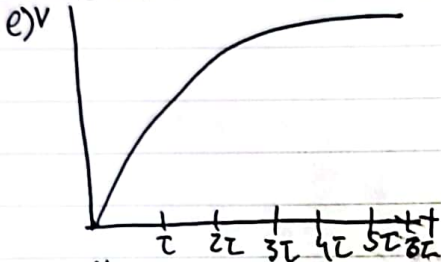c)  $i = 0 \rightarrow$  open circuit


$$d) V_C(t) = V_s (1 - e^{-\frac{t}{\tau}}) = 10 (1 - e^{-\frac{t}{0.02}})$$



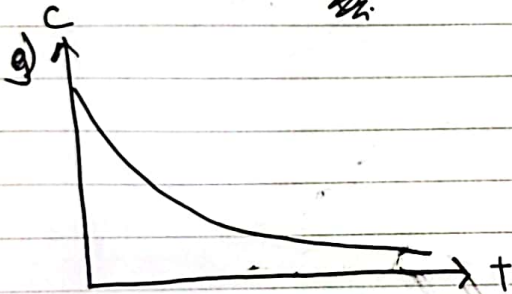
$$f) i(t) = \frac{V_s - V_C(t)}{R} = \frac{10 - 10(1 - e^{-\frac{t}{0.02}})}{200} = 0.05 e^{-\frac{t}{0.02}} \text{ A}$$







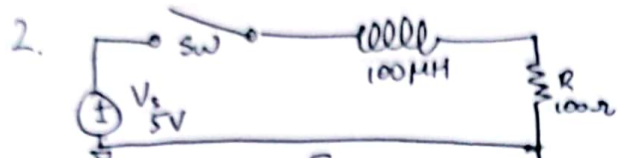

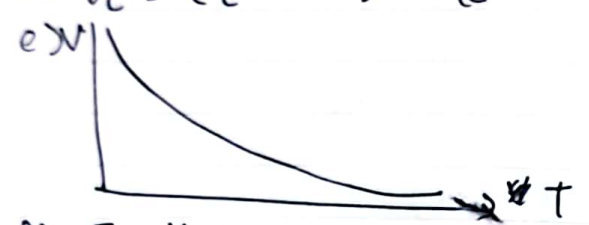- a)  $i(0) = \frac{5}{100} = 0.05 \text{ A}$   
 b)  $\tau = \frac{L}{R} = \frac{100 \mu\text{H}}{100 \Omega} = 1 \mu\text{s}$   
 c)  $i = 500 \text{ A}$   
 d)  $V_L = (e^{-Rt/L}) = (e^{-100t/0.001})$



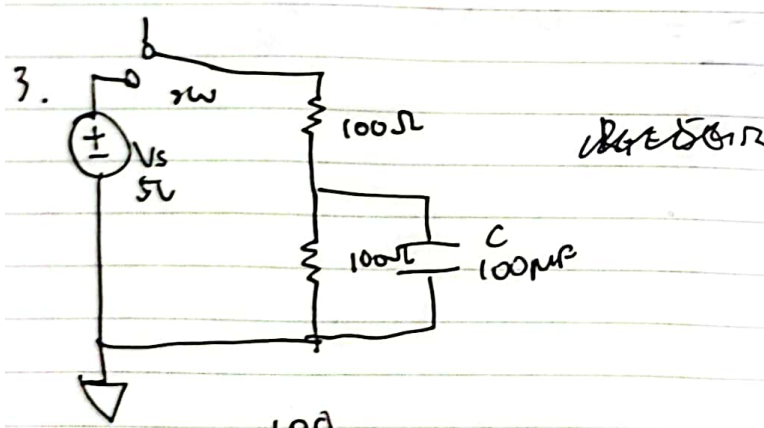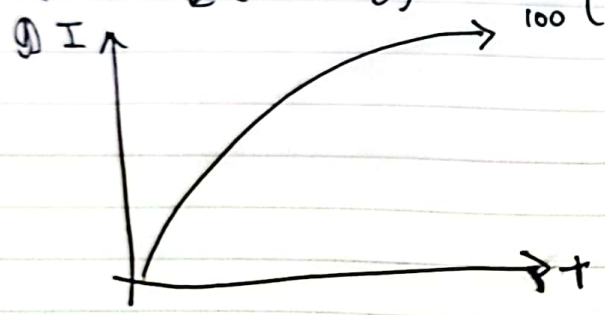
f)  $I = \frac{V}{R} (1 - e^{-\frac{Rt}{L}}) = \frac{5}{100} (1 - e^{-\frac{100t}{0.001}})$




- a)  $5 \times \frac{100}{100+100} = 2.5 \text{ V}$   
 b)  $-2.5 \text{ V}$   
 c)  $5\tau = 5RC = 100 \mu\text{F} \times 50 \times 5 = 0.025 \text{ s}$

d)  $V(t) = V_s (1 - e^{-\frac{t}{\tau}}) = 2.5 (1 - e^{-\frac{t}{0.025}})$

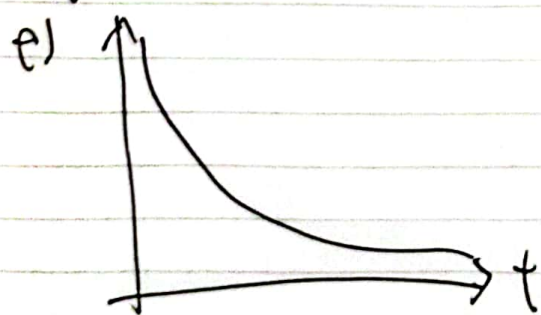e)  $2.5 (1 - e^{-\frac{t}{0.025}})$   $t = 0.025 \text{ s}$



4.

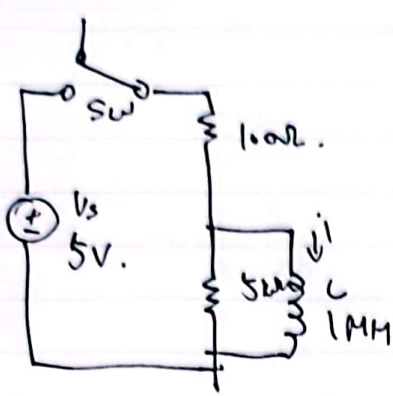

$$a) I = \frac{5}{100} = 0.05 A.$$

$$b) I = -0.05 A.$$

$$c) V = IR = -0.05 \times 5k\Omega = -250V$$

$$d) V = 5000 \times i(t)$$

$$i(t) = I_0 e^{-\frac{t}{\tau}}$$

$$\tau = \frac{L}{R} = \frac{10^{-6}}{5000} = 2 \times 10^{-10} s$$

$$V(t) = -250 e^{-5 \times 10^9 t} V.$$

