

# EEP1 ELogBook – Week 8

AXXXXXXX - Brians Tjipto Meidianto

## Studio

### Activity 1a:

1. Question 1
  - a. Initial Current of C1:  
$$((10 - V) / 80) + ((10 - V) / 100) = (V / 20) + (V / 400)$$
$$V = 3$$
$$I_c = I_2 - I_1 = (3 / 20) - (7 / 80) = 0.0625A$$
  - b. Steady state voltage of C1:  
$$V_{ba} = 10 * (100 / (100 + 400)) - 10 * (80 / (80 + 20)) = -6V$$
2. Question 2
  - a. Initial current of L1:  
 $I = 0A$ , open circuit
  - b. Steady state voltage of L1:  
 $V = 0V$ , Short circuit
3. Warm up exercise 1:
  - a. At  $t = 0^+$ 
    - i. Current:  $0A$
    - ii. Capacitor voltage:  $0V$
    - iii. Inductor voltage:  $5V$
  - b. Steady state
    - i. Current:  $0A$
    - ii. Capacitor voltage:  $5V$
    - iii. Inductor voltage:  $0V$
4. Warm up exercise 2:
  - a. At  $t = 0^+$ 
    - i. Capacitor current:  $0A$
    - ii. Capacitor voltage:  $0V$
    - iii. Inductor current:  $0A$
    - iv. Inductor voltage:  $12V$
  - b. Steady state
    - i. Capacitor current:  $0A$
    - ii. Capacitor voltage:  $R_2 / (R_1 + R_2) * V_1 = 22k\Omega / (21k\Omega + 22k\Omega) * 12 = 6.13 V$
    - iii. Inductor current:  $V_1 / (R_1 + R_2) = 12 / (21k\Omega + 22k\Omega) = 0.28 mA$
    - iv. Inductor voltage:  $0V$

### Activity 1b:

1. Capacitor:
  - a. Receiving energy:
    - i. The capacitor voltage will gradually increase over time, following an exponential growth curve.
    - ii. The capacitor current will be initially high and decrease exponentially toward zero.
  - b. Giving out energy:

- i. The capacitor voltage will gradually increase over time, following an exponential growth curve.
- ii. The capacitor current will be initially high and decrease exponentially toward zero.

## 2. Inductor:


### a. Receiving energy:

- i. The capacitor voltage will gradually increase over time, following an exponential growth curve.
- ii. The capacitor current will be initially high and decrease exponentially toward zero.


### b. Giving out energy:

- i. The capacitor voltage will gradually increase over time, following an exponential growth curve.
- ii. The capacitor current will be initially high and decrease exponentially toward zero.

## Activity 1c:

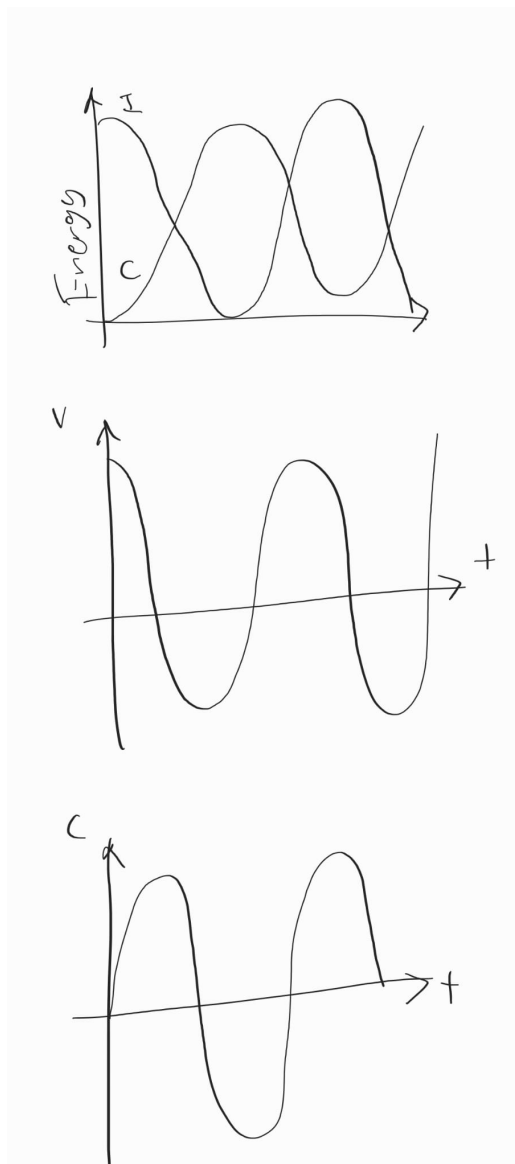

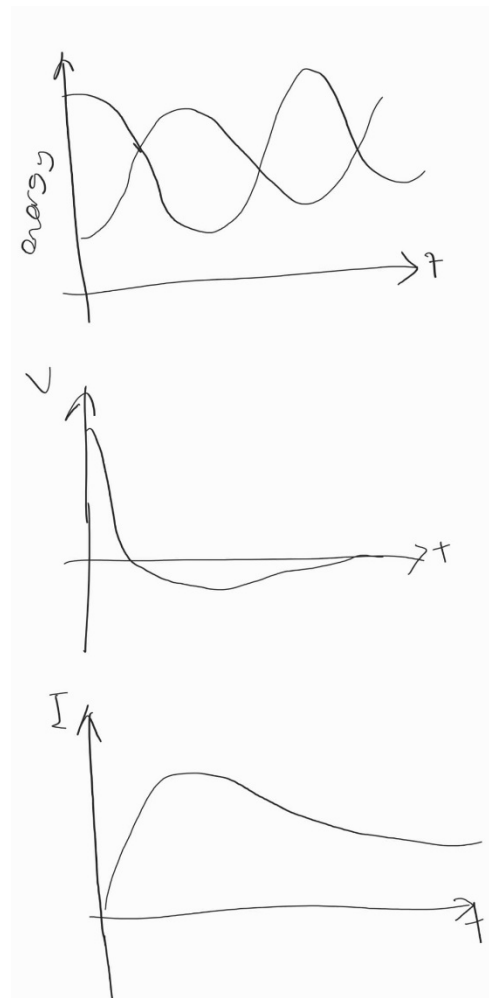Once you add an extra resistor, the initial condition will change,  $V_c(0) = V_0$ , while  $I(0) = I_0$ .





## Activity 2:

$$1. \quad \omega_n = \frac{1}{\sqrt{(1 \times 10^{-9})(1 \times 10^{-3})}} = 1 \times 10^6 \text{ rad/s}$$

$$\zeta = \frac{220}{2} \sqrt{\frac{1 \times 10^{-9}}{1 \times 10^{-3}}} = 0.11$$

$$\omega_d = 1 \times 10^6 \sqrt{1 - 0.11^2} = 0.9939 \times 10^6$$
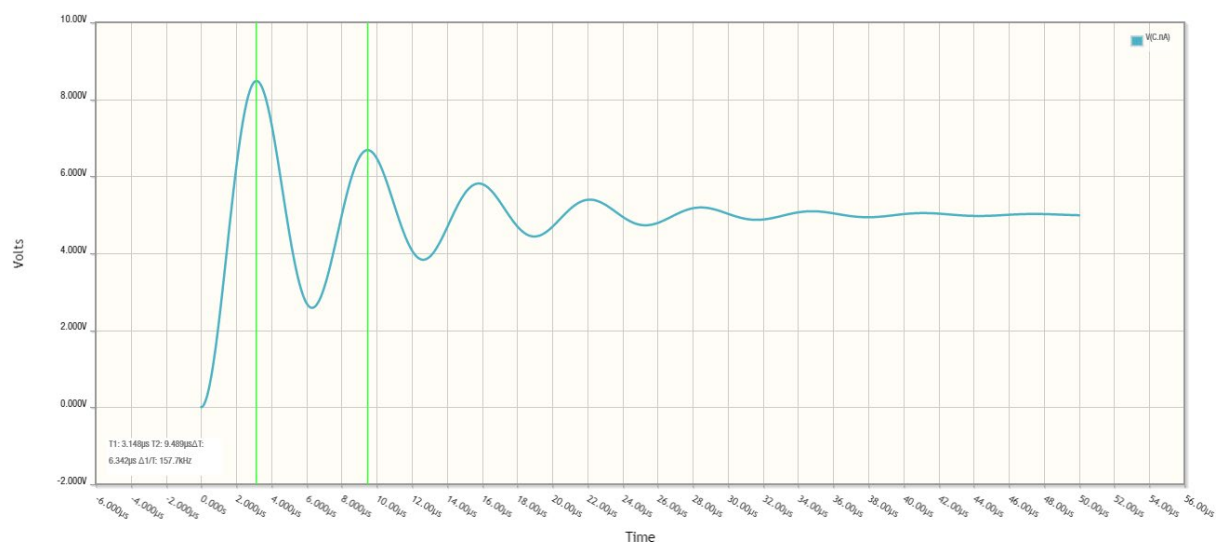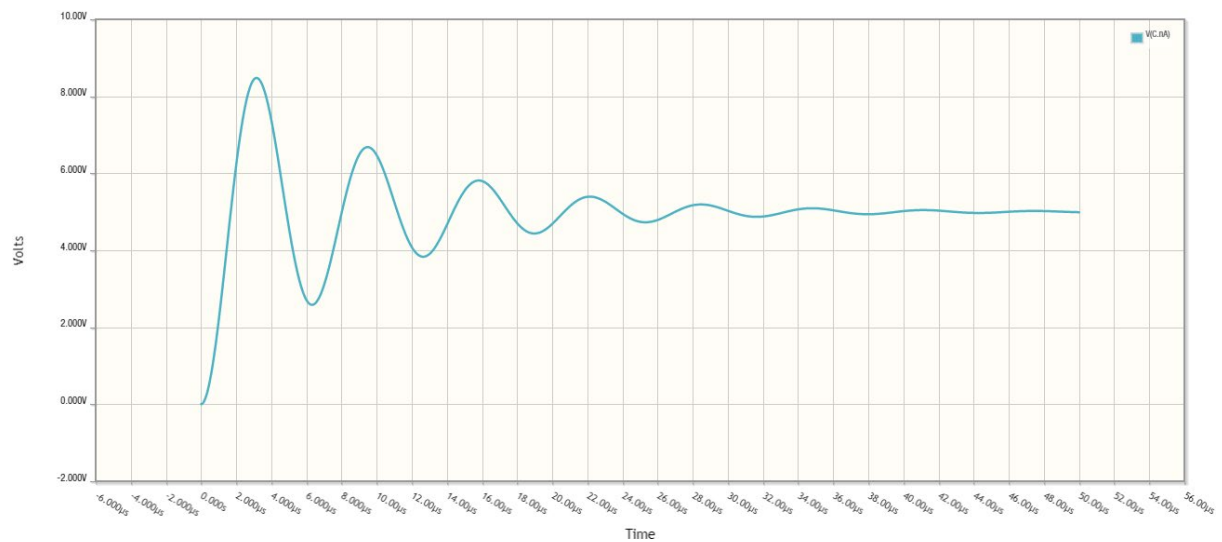
$$2. \quad R_{cd} = 2 \sqrt{\frac{1 \times 10^{-3}}{1 \times 10^{-9}}} = 2 \times 10^3 \Omega$$




Time difference: 6.342us


$$2\pi f = 2\pi/T$$

$$2\pi f = 990726.2$$
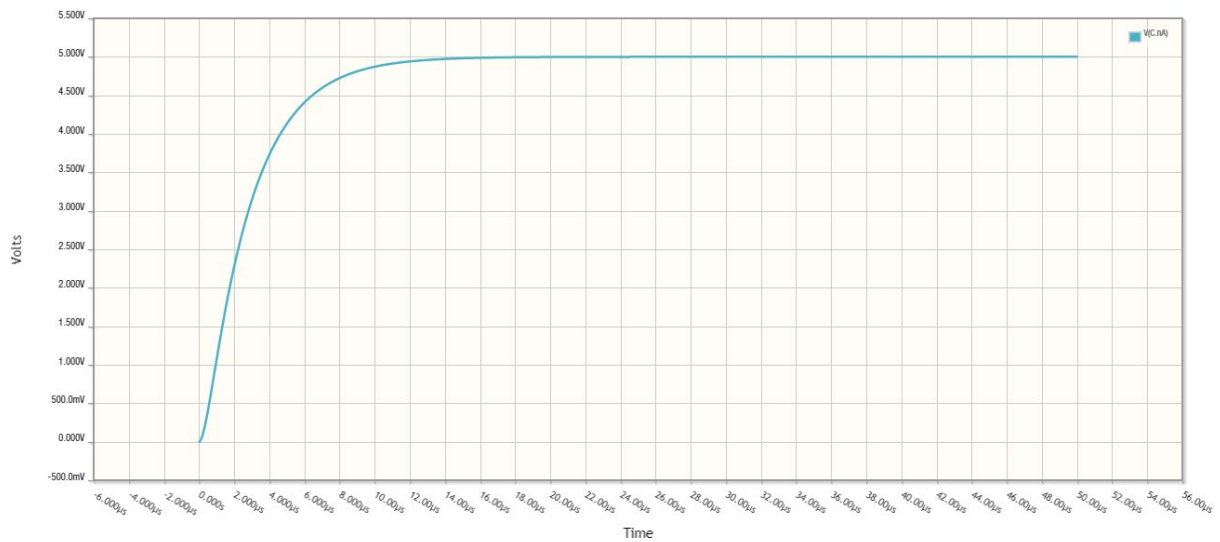
$$f = 157679\text{Hz} = 157.7\text{kHz}$$


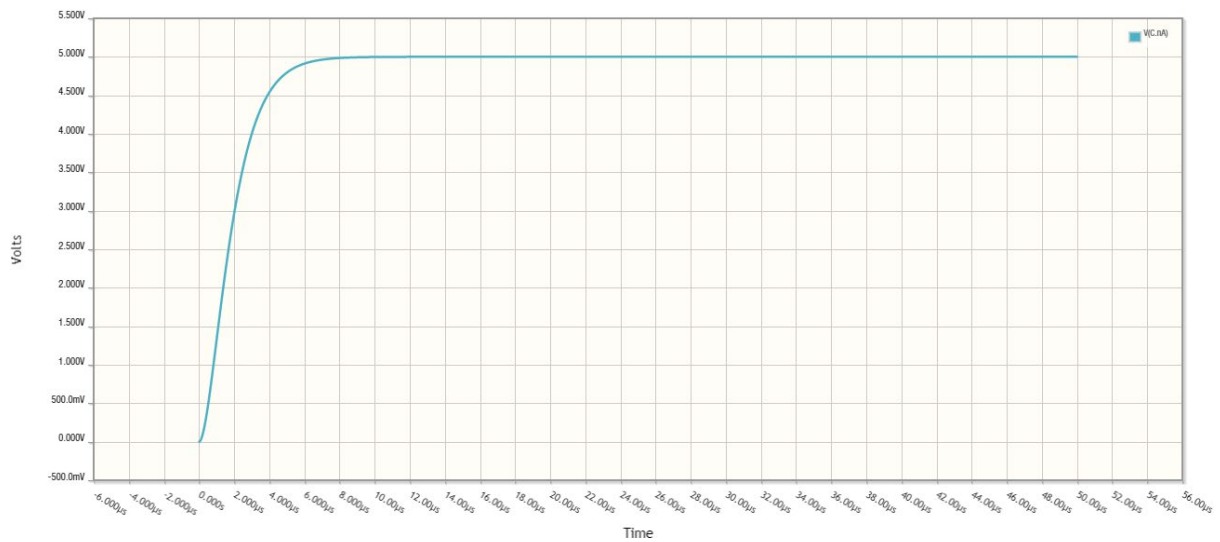
$$\zeta = \frac{2000}{2} \sqrt{\frac{1 \times 10^{-9}}{1 \times 10^{-3}}} = 1 - \text{Critically Damped}$$



$$\zeta = \frac{3000}{2} \sqrt{\frac{1 \times 10^{-9}}{1 \times 10^{-3}}} = 1.5 - \text{Over Damped}$$





The value of damping ratio significantly influences the nature of the response in a dynamic system; a  $\zeta$  of 1 indicates critical damping, resulting in a well-balanced response without oscillations,  $\zeta > 1.5$  leads to overdamping, causing sluggish and slow responses, while a low  $\zeta$  of 0.11 signifies underdamping, leading to oscillatory and potentially unstable responses.

## Lab

### Activity 1

Length	Extension	Weight
6.4	0	0
8.1	1.7	0.25
10	1.9	0.5

Gradient is 3.8

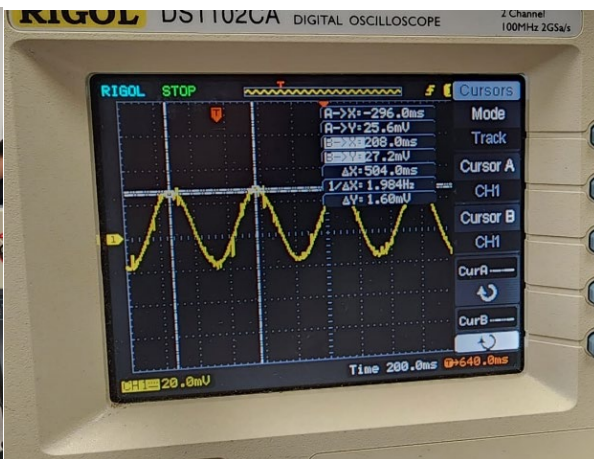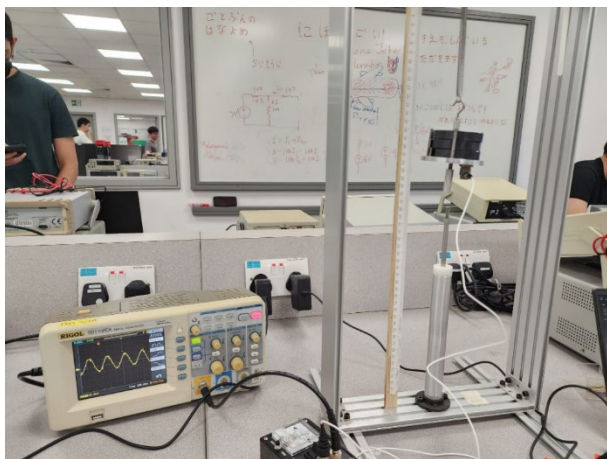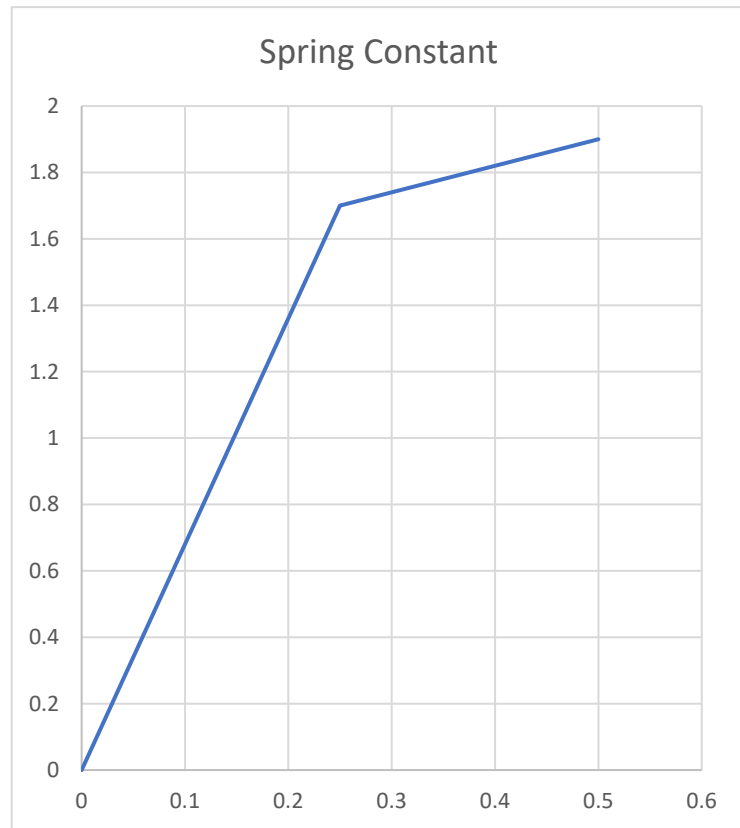
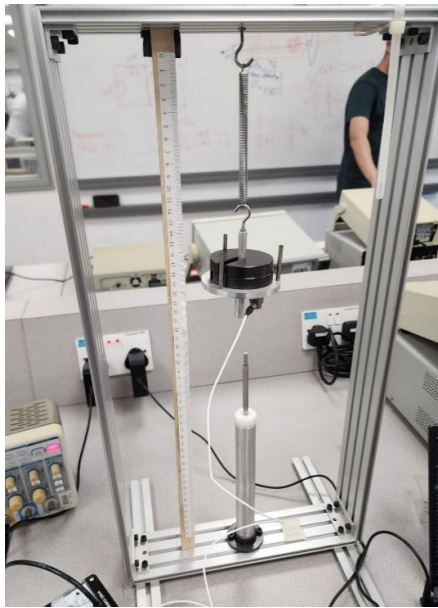


$$T_n = 504\text{ms}$$

$$W_n = 2\pi/T_n$$

$$W_n = 12.5 \text{ rad/s}$$
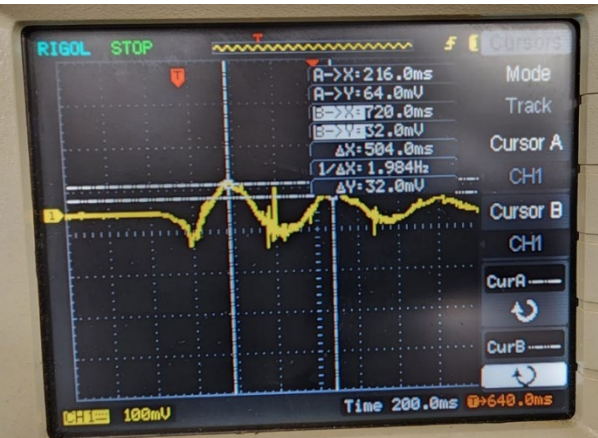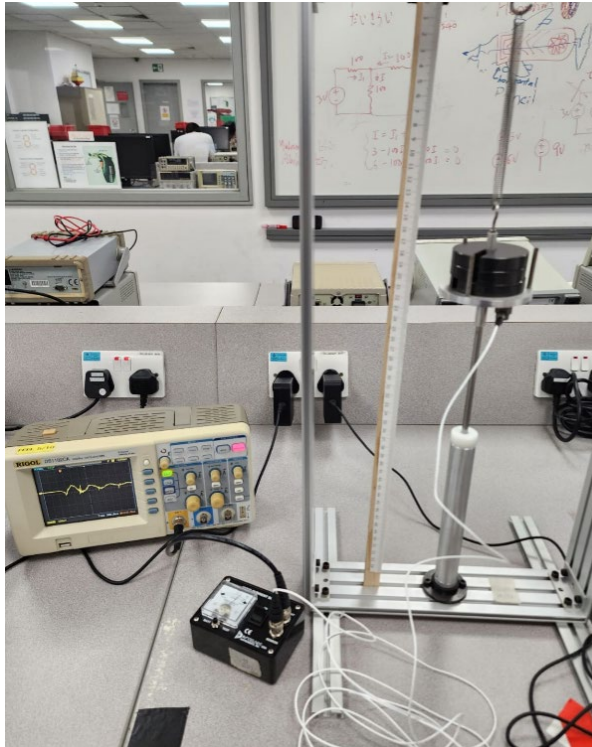
$$W_{n,th} = \sqrt{\frac{k}{m}} = \sqrt{\frac{3.8}{0.75}} = 2.25$$



$$T_d = 504\text{ms}$$

$$\omega_d = 2\pi/T_d$$

$$\omega_d = 12.5\text{ rad/s}$$

$$\omega_d = 12.5\sqrt{1 - \zeta^2} = 12.5$$

$$\zeta = 0$$


$$\zeta = \frac{c}{2\sqrt{mk}} = \frac{c}{2\sqrt{0.75 * 3.8}} = 0, c = 0$$

The machine is not working as expected, and it resulted in the damping ratio being 0, theoretically, the damping ratio should be a bit larger than 0, and not 0.



## Activity 2

Resistor	Capacitor	Inductor	$\zeta$	$\omega_n$	$\omega_d$
220	0.000000001	0.001	0.11	1000000	993931.5872
1000	0.000000001	0.001	0.5	1000000	866025.4038
2000	0.000000001	0.001	1	1000000	-
3300	0.000000001	0.001	1.65	1000000	-

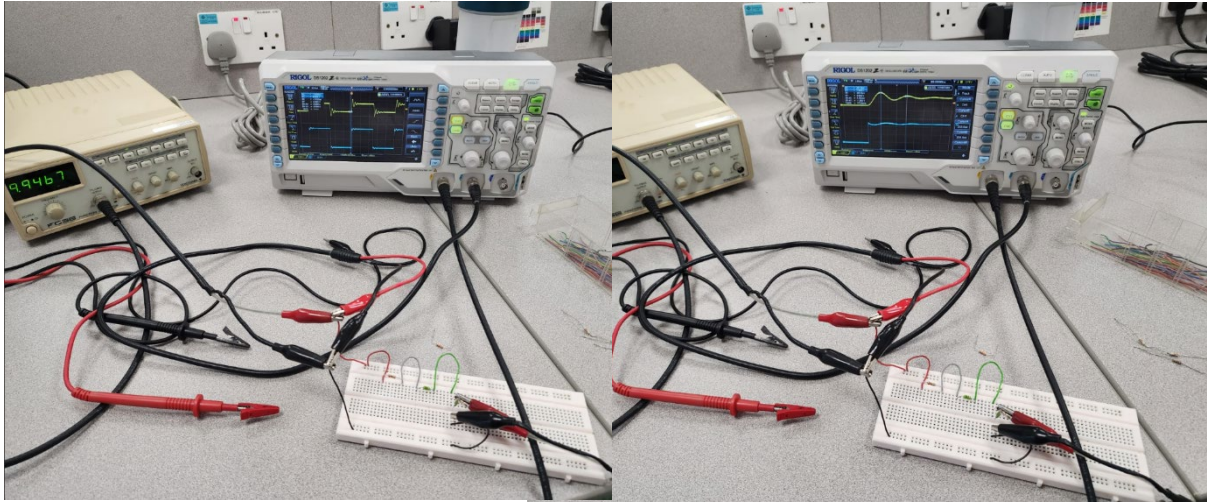


$$T = 5.880 \text{ us}$$


$$T = 2\pi/f$$

$$5.880 \cdot 10^{-6} = 2\pi/f$$

$$f = 1068568.9 = 1068.6 \text{ kHz}$$

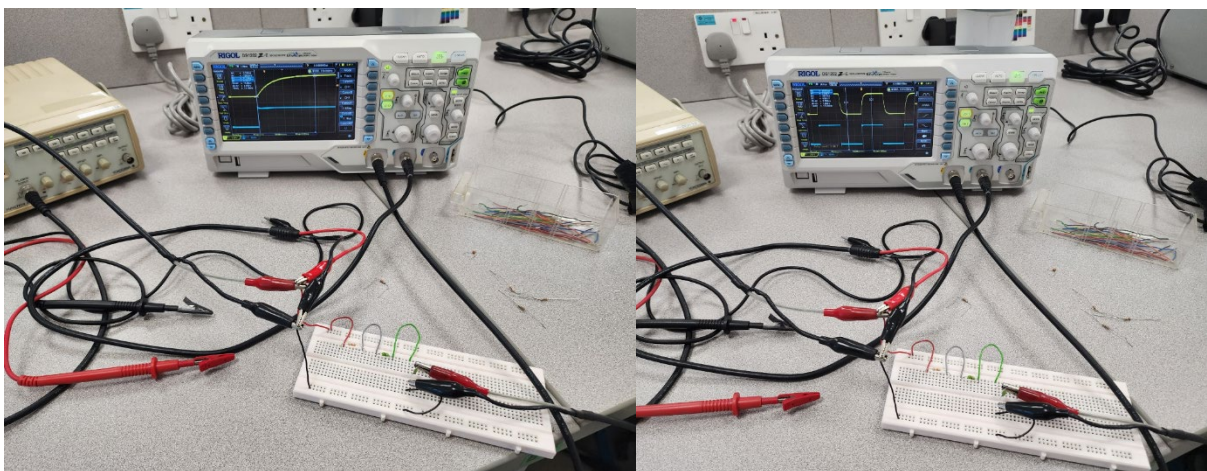
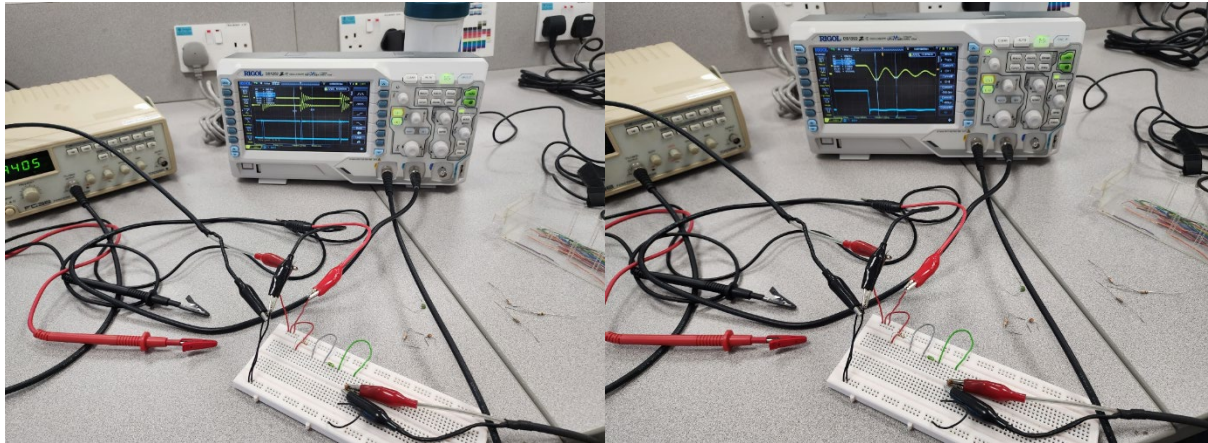
$$\text{Time taken to reach steady state} = 13.48 \text{ us}$$



$$T = 2.280\mu\text{s}$$

$$T = 2\pi/f$$

$$2.280 \cdot 10^{-6} = 2\pi/f$$

$$f = 2755783\text{Hz} = 275.6\text{ kHz}$$

The damping of the 220 Ohm is lowest meaning it is underdamped, while the 3300 Ohm, one shows it being overdamped. The one with the lower Capacitor, had a lower value for  $\zeta$ , making it more underdamped, and had a lower frequency compared to the 1000pF one.