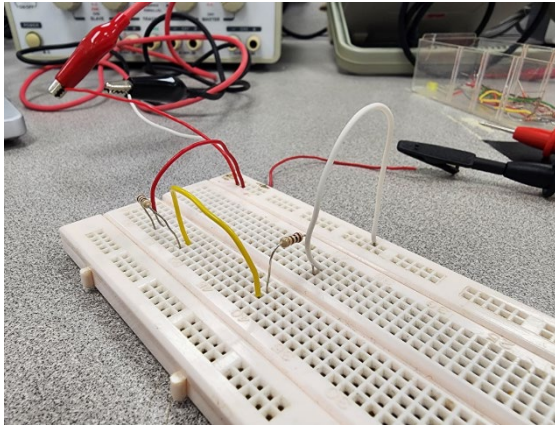


EEP1 ELogBook – Week 4


AXXXXXXX - Brians Tjipto Meidianto

Lab


Activity 1




1. $V1 = 2.52V$
2. $V2 = 2.53V$
3. $Vs = V1 + V2 = 2.52 + 2.53 = 5.05V$
4. Conclusion: The KVL checks out stating that the sum of a closed loop path is 0.

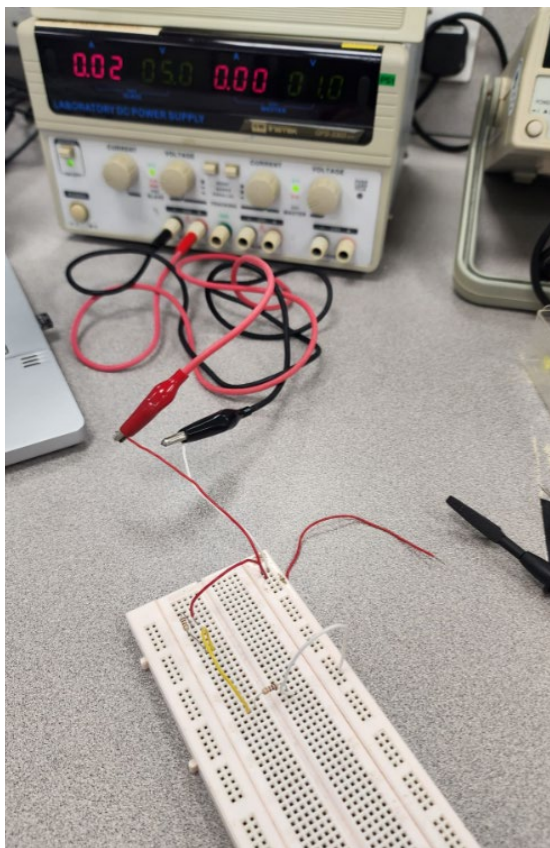

Activity 2


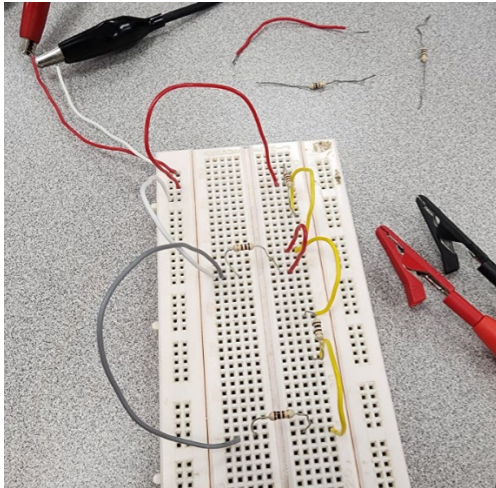


1. $I_1 = 29.3 \text{ mA}$
2. $I_2 = 19.6 \text{ mA}$
3. $I_3 = 9.8 \text{ mA}$
4. $I_1 = I_2 + I_3 = 19.6 + 9.8 = 29.4 \text{ mA}$
5. Conclusion: The KCL checks out stating that the sum enters a node is equal to the sum leaving the node.

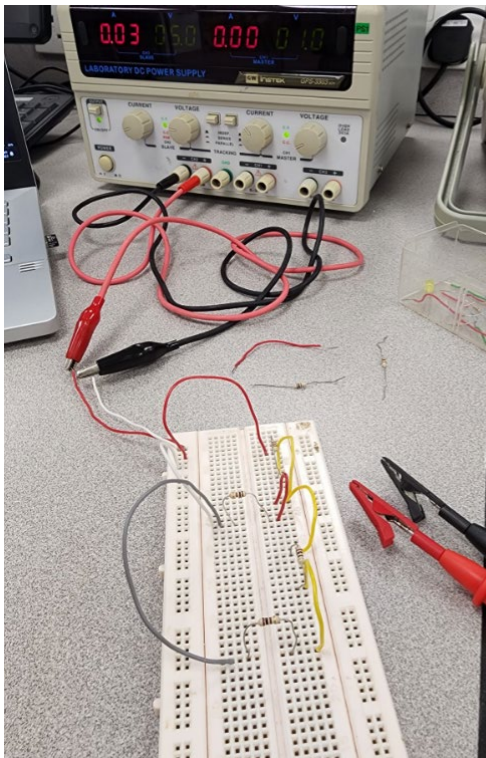


Activity 3


1. $i = 30.2\text{mA}$

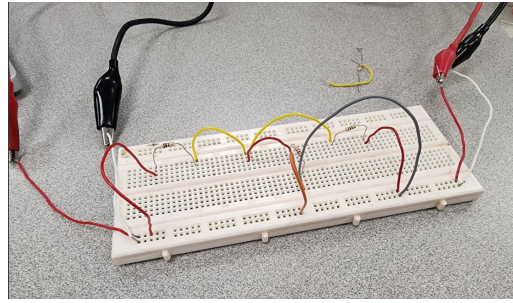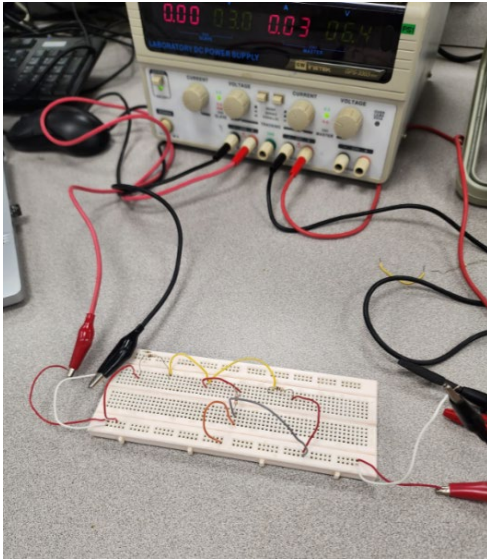

2. $i_1 = 9.5\text{mA}$

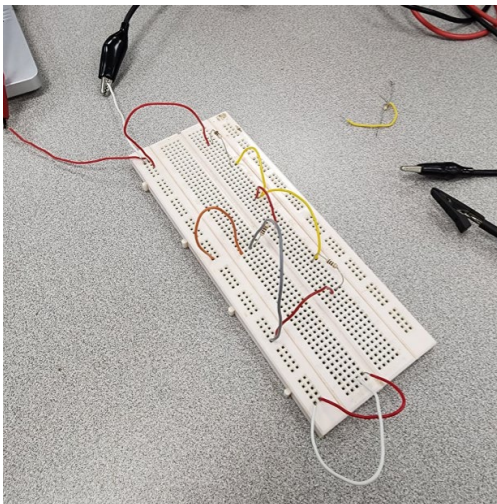


3. $i_2 = 20.6\text{mA}$

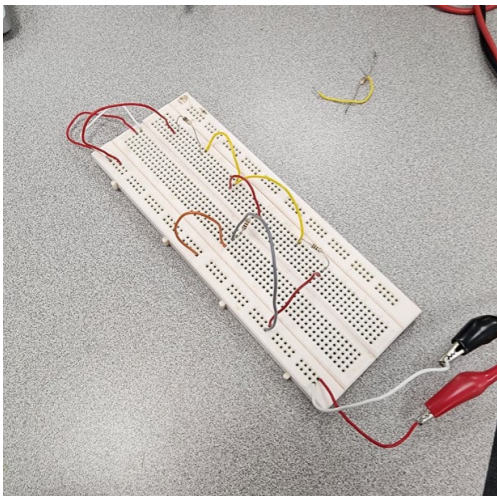

4. $i = i_1 + i_2 = 9.5 + 20.6 = 30.1\text{mA}$
5. The Superposition Theorem checks out as the sum of i_1 and i_2 is 30.1mA , while the i from the total measurement is 30.2mA .

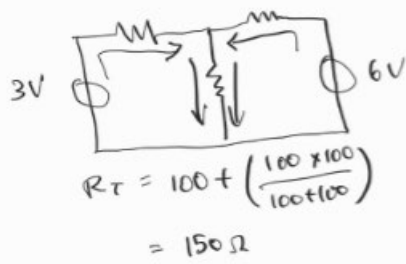6. Analytical verification of superposition principle



$$I_{T1} = \frac{V_1}{R_T} = \frac{3}{150} = 20 \text{ mA}$$


$$i_1 = \frac{R_2}{R_1 + R_2} \times I_{T1}$$
$$= \frac{100}{100 + 100} \times 20 = 10 \text{ mA} //$$

$$I_{T2} = \frac{V_2}{R_T} = \frac{6}{150} = 40 \text{ mA}$$

$$i_2 = \frac{R_3}{R_2 + R_3} \times I_{T2}$$
$$= \frac{100}{100 + 100} \times 40 = 20 \text{ mA} //$$

$$i = i_1 + i_2 = 10 + 20$$
$$= 30 \text{ mA} //$$

Activity 4

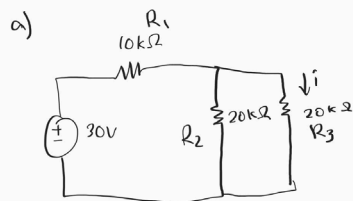


$$R_T = 10k + \left(\frac{20k \times 20k}{20k + 20k} \right)$$

$$= 20k$$

$$I_T = \frac{V_S}{R_T} = \frac{30}{20k} = 1.5mA$$

$$I_{R_3} = \frac{R_2}{R_2 + R_3} \times I_T$$

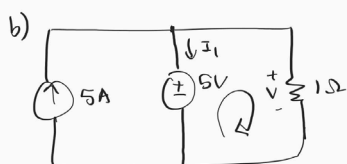
$$= \frac{20}{20 + 20} \times 1.5 = 0.75mA$$



$$V = 5 \times 1 = 5V$$

$$i_1 = \frac{0}{0 + 1} \times 5A$$

$$= 0A$$

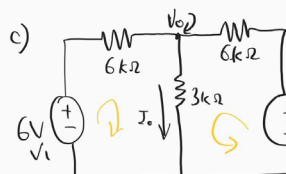

$$R_T = 6k + \left(\frac{6k \times 3k}{6k + 3k} \right) = 8k\Omega$$

$$I_{V_1} = \frac{6}{8k} = 0.75mA$$

$$I_{01} = 0.75 \times \frac{6k}{3k + 6k} = 0.5mA$$



$$I_{V_2} = \frac{3}{8k} = 0.375mA$$

$$I_{02} = 0.375 \times \frac{6k}{3k + 6k} = 0.25mA$$

$$I_{0T} = 0.5 + 0.25 = 0.75mA$$

$$V_0 = 0.75mA \times 3k\Omega$$

$$= 2.25V$$

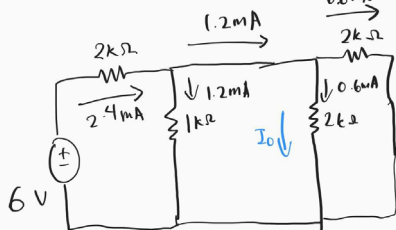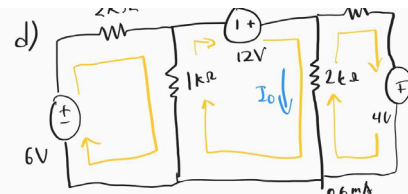

$$R_T = 2k + \left(\frac{1}{\frac{1}{1k} + \frac{1}{2k} + \frac{1}{2k}} \right)^{-1}$$


$$= 2.5k\Omega$$

$$R = \left(\frac{1}{2k} + \frac{1}{2k} \right)^{-1} = 1k\Omega$$

$$I_{V_T} = \frac{6}{2.5} = 2.4mA$$

$$I = \left(\frac{1}{1+1} \right) \times 2.4 = 1.2mA$$
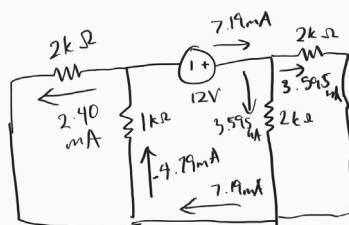
$$I = \left(\frac{2}{2+2} \right) \times 1.2 = 0.6mA$$



$$R_T = \left(\frac{2 \times 2}{2+2} \right) + \left(\frac{2 \times 1}{2+2} \right)$$



$$= 1.67k\Omega$$

$$I_{R_T} = \frac{12}{1.67} = 7.19mA$$

$$I = 7.19 \times \left(\frac{2}{2+2} \right) = 3.595mA$$

$$I = 7.19 \times \left(\frac{2}{1+2} \right) = 4.79mA$$
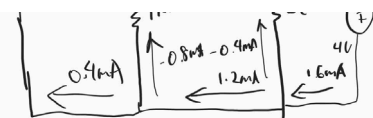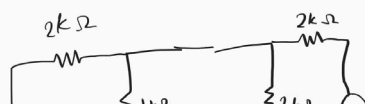
$$I = 7.19 \times \left(\frac{1}{1+2} \right) = 2.40mA$$



$$R_T = \left(\frac{1}{2} + \frac{1}{1} + \frac{1}{2} \right)^{-1} + 2 = 2.5k\Omega$$

$$I_{R_T} = \frac{4}{2.5} = 1.6mA$$

$$R = \left(\frac{1 \times 2}{1+2} \right)^{-1} = 0.67k\Omega$$

$$I = \left(\frac{0.67}{0.67+2} \right) \times 1.6 = 0.40mA$$

$$I = \left(\frac{2}{0.67+2} \right) \times 1.6 = 1.20mA$$

$$I = \left(\frac{2}{1+2} \right) \times 1.2 = 0.8mA$$

$$I = \left(\frac{1}{1+2} \right) \times 1.2 = 0.4mA$$

$$I_0 = 0.6 + 3.595 + (-0.4)$$

$$= 3.795mA$$


$$V_1 = 6V$$

$$V_2 = (1.2 \times 1) + (-4.79 \times 1) + (-0.8 \times 1)$$

$$= -4.39V$$

$$V_3 = (0.6 \times 2) + (3.595 \times 2) + (-0.4 \times 2)$$

$$= 7.59mA$$

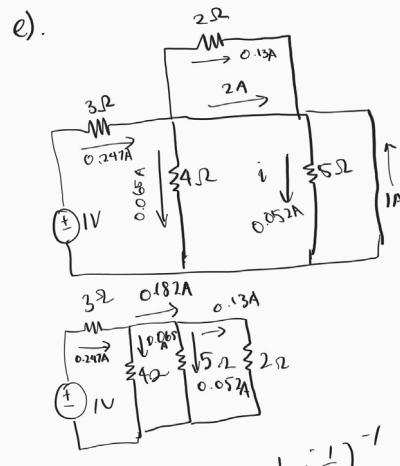

$$\left(\frac{1}{1} + \frac{1}{2} + \frac{1}{2} \right)^{-1}$$

$$R_T = 3 + \left(\frac{1}{\frac{1}{4} + \frac{1}{5}} \right)$$

$$= 4.05 \Omega$$

$$R = \frac{5 \times 2}{5+2} = 1.43 \Omega$$

$$I_{R1} = \frac{1}{4.05} = 0.247 A$$

$$I = 0.247 \times \left(\frac{1.43}{1.43+4} \right)$$

$$= 0.065 A$$

$$I = 0.247 \times \left(\frac{4}{4+1.43} \right)$$

$$= 0.182 A$$

$$I = 0.182 \times \left(\frac{2}{5+2} \right)$$

$$= 0.052 A$$

$$I = 0.182 \left(\frac{5}{5+2} \right)$$



$$= 0.13 A$$

$$v = 2 + (-1) + (-0.052)$$

$$= 0.948 A //$$

$$v_2 = 0.948 \times 5$$

$$= 4.74 V //$$

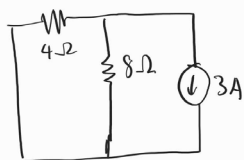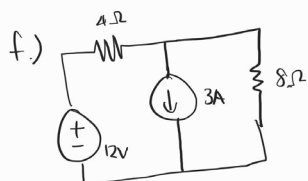

$$R_T = \frac{4 \times 8}{4+8} = 2.67$$

$$V_{3A} = 2.67 \times 3$$

$$= 8.01 V //$$



$$V_{4\Omega} = \frac{4}{4+8} \times 12 = 4 V //$$

$$V = V_{12V} + V_{3A}$$

$$= 4 + 8 = 12 V //$$

Circuit analysis practice problems

- Using KVL and KCL, determine the unknown currents I_C , I_D and the unknown voltages V_B and V_D in the circuit given in Fig.1.

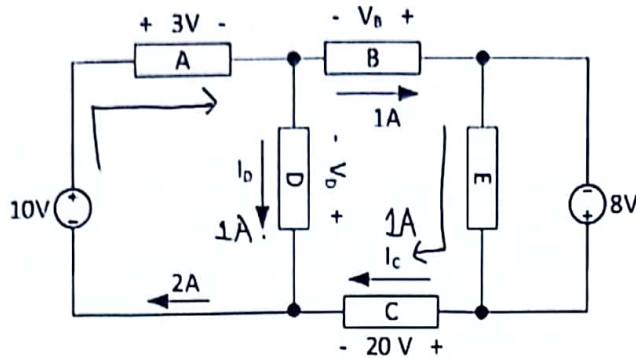


Figure 1: KVL KCL practice problem

- For the circuit given in Fig.2,

- write the KVL equations for the loop1 and loop2.
- write the KCL equations for the Node 2 and the super-node.

in terms of the unknown branch currents, and given voltage and current sources.

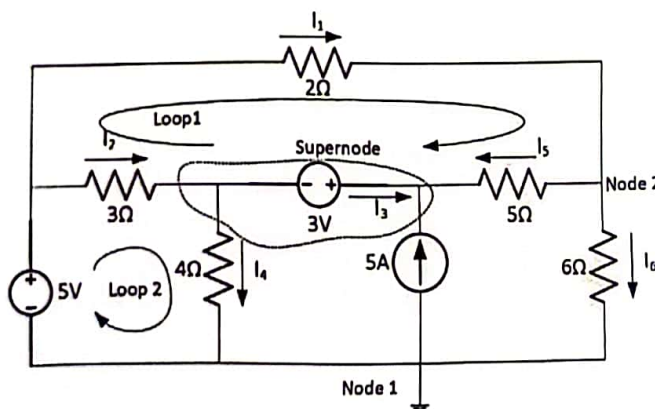


Figure 2: KVL KCL practice problem

$$\begin{aligned}
 I_C &= 1A // \\
 I_D &= 2 - 1 = 1A // \\
 KVL &= 3 + V_D + 20 - 10 = 0. \\
 V_D &= -7V // \\
 KVL &= -8 + 20 + 3 + V_B + 10 \\
 &= 5V //
 \end{aligned}$$

$$\begin{aligned}
 2.a) \quad & \text{KVL} = I_1 + I_5 + 3V - I_2 = 0. \\
 & \text{KVL} = -2I_1 + 5I_2 + 3V - 3I_2 = 0 // \\
 & -5V + I_2 + I_4 = 0. \\
 & -5V + 3I_2 + 4I_4 = 0 //
 \end{aligned}$$

$$\begin{aligned}
 b) \quad & KCL = I_1 = I_5 + I_6 // \\
 & I_2 + I_5 + 5A = I_4
 \end{aligned}$$

3. Using series/parallel rule, determine the equivalent resistance seen by the source in Fig.3. Hence, find the current I drawn from the source.

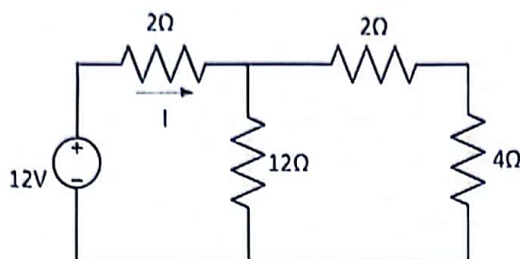


Figure 3: Equivalent resistance practice problem

$$R_T = \left(\frac{12 \times 6}{12 + 6} \right) + 2 = 6 \Omega$$

$$I = \frac{V}{R} = \frac{12}{6} = 2A //$$

4. Branch current method: use KVL/KCL to write three independent equations containing the unknown branch currents I_1 , I_2 and I_3 in the circuit given in Fig.4. Solve the linear system of equations.

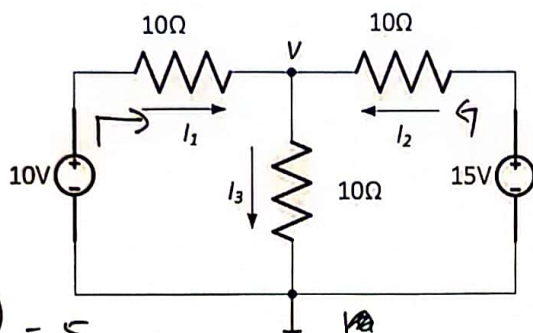


Figure 4: Branch current practice problem

$$KCL = I_1 + I_2 = I_3$$


$$KVL = 10 + 10I_1 + 10I_3 = 0$$

$$KVL = 15 + 10I_2 + 10I_3 = 0$$

$$\left(\frac{10 \times 10}{10 + 10} \right) = 5$$

$$5 + 10 = 15 \Omega$$

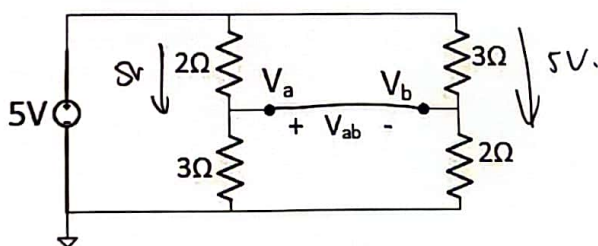5. Using voltage divider principle, determine voltages V_a and V_b in Fig.5. Hence, find the voltage V_{ab} .



$$V_a = \frac{2}{3+2} \times 5 = 2$$

$$V_b = \frac{3}{3+2} \times 5 = 3$$

$$V_{ab} = V_b - V_a = 3 - 2 = 1V //$$


10V	15V
$I_1 = \frac{10}{15} = \frac{2}{3}$	$I_2 = \frac{15}{15} = 1$
$I_3 = \frac{10}{20} \times \frac{2}{3} = \frac{1}{3}$	$I_1 = 0.5$
$I_2 = \frac{1}{3}$	$I_3 = 0.5$

$$\therefore I_1 = \frac{2}{3} - 0.5 = \frac{1}{6}A //$$


$$I_2 = 1 - \frac{1}{3} = \frac{2}{3}A //$$

$$I_3 = \frac{1}{3} + 0.5 = \frac{5}{6}A //$$

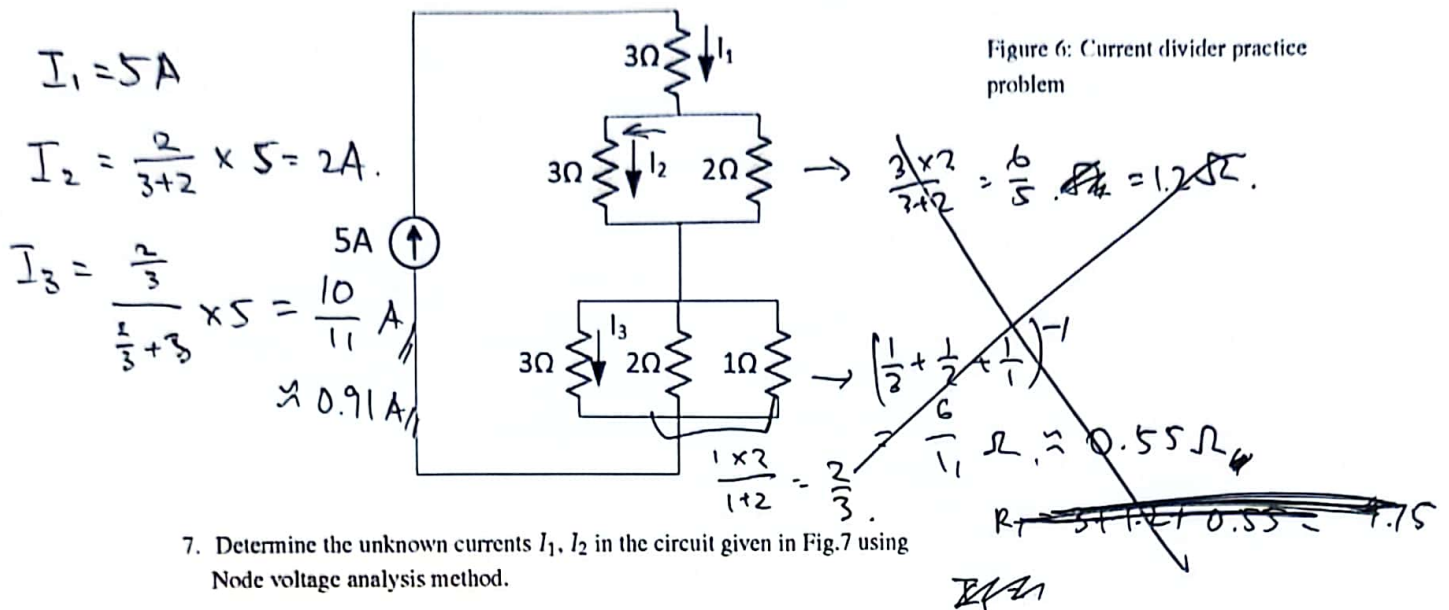
6. Using current divider principle, determine currents I_1 , I_2 and I_3 in Fig.6.




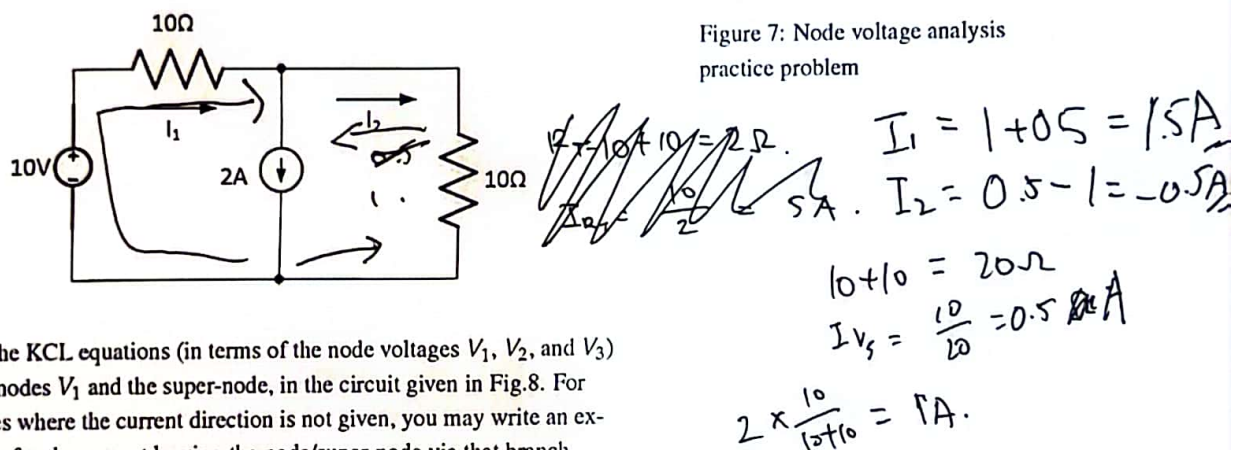7. Determine the unknown currents I_1 , I_2 in the circuit given in Fig.7 using Node voltage analysis method.



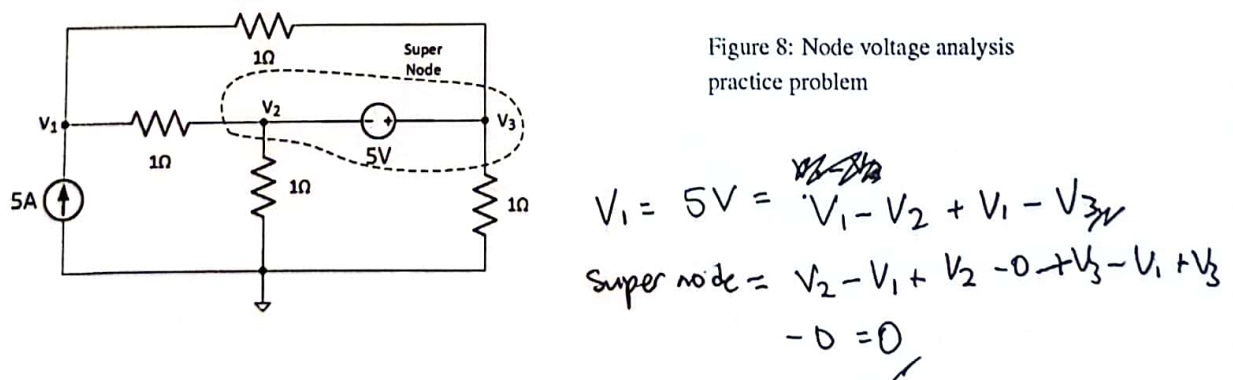8. Write the KCL equations (in terms of the node voltages V_1 , V_2 , and V_3) for the nodes V_1 and the super-node, in the circuit given in Fig.8. For branches where the current direction is not given, you may write an expression for the current leaving the node/super-node via that branch.



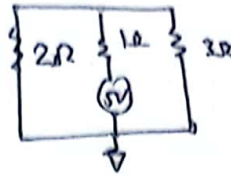

9. Determine the values of currents I_1 , I_2 and I_3 for the circuit in Fig.9 using node voltage analysis method.

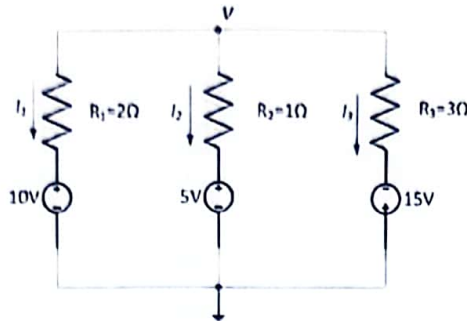


Figure 9: Node voltage analysis practice problem

$$10V \rightarrow R_T = \left(\frac{1}{3} + \frac{1}{1}\right)^{-1} + 2 = \frac{1}{4} \text{ A}$$

$$I_{R1} = \frac{10}{1/4} = 40 \text{ A}$$

$$I_{R2} = \frac{3}{3+1} \times \frac{40}{11} = \frac{30}{11} \text{ A}$$

$$I_{R3} = \frac{1}{3+1} \times \frac{40}{11} = \frac{10}{11} \text{ A}$$

10. Determine the value of voltage V_{R1} in the circuit given in Fig.10 using node voltage analysis method.

$$5V \rightarrow R_T = \left(\frac{1}{2} + \frac{1}{3}\right)^{-1} = \frac{6}{5} \Omega$$

Figure 10: Node voltage analysis practice problem

$$R_T = \left(\frac{2 \times 3}{2+3}\right) + 1 = 2.2 \Omega$$

$$I_1 = \frac{3}{2+3} \times \frac{25}{11} = \frac{15}{11} \text{ A}$$

$$I_2 = \frac{5}{2.2} = \frac{25}{11} \text{ A}$$

$$I_3 = \frac{2}{2+3} \times \frac{25}{11} = \frac{10}{11} \text{ A}$$

$$15V \rightarrow R_T = \left(\frac{2 \times 1}{2+1}\right) + 3 = \frac{11}{3}$$

$$I_1 = \frac{1}{1+2} \times \frac{45}{11} = \frac{15}{11} \text{ A}$$

$$I_2 = \frac{2}{1+2} \times \frac{45}{11} = \frac{30}{11} \text{ A}$$


$$I_3 = \frac{15}{11/3} = \frac{45}{11} \text{ A}$$

$$\therefore I_1 = \frac{40}{11} - \frac{15}{11} - \frac{15}{11} + \frac{15}{11} = -\frac{40}{11} \text{ A}$$

$$I_2 = -\frac{30}{11} - \frac{25}{11} + \frac{30}{11} = -\frac{25}{11} \text{ A}$$

$$I_3 = \frac{10}{11} + \frac{10}{11} + \frac{45}{11} = \frac{65}{11} \text{ A}$$
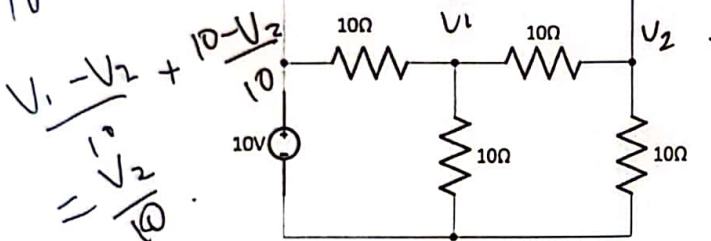
$$\frac{10-V}{10} = \frac{V_1}{10} + \frac{V_1+V_2}{10}$$



$$\frac{V_1 - V_2}{10} + \frac{10-V_2}{10} = \frac{V_2}{10}$$

Show your detailed step-by-step workings for all circuit analysis problems in your eLogbook. This will help you refer to them in future for revision.

$$V_2 = 5V \quad E\text{-logbook}$$

$$V_1 = 5$$

$$V_{R1} = 10 - 5 = 5V$$

$$R_T = \frac{20 \times 10}{20+10} = \frac{20}{3} \Omega$$

$$I_{R_T} = \frac{10}{25/4} = 1.6 \text{ A}$$

$$1.6 \times \frac{50}{3} =$$

Take-home extra practice problems

- (a) Find equivalent resistance of the circuit given in Fig.11.

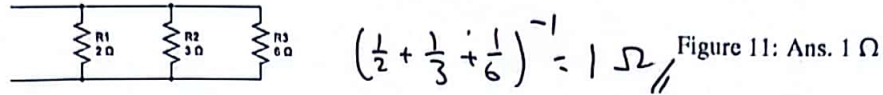


Figure 11: Ans. 1 Ω

- (b) Find equivalent resistance of the circuit given in Fig.12.

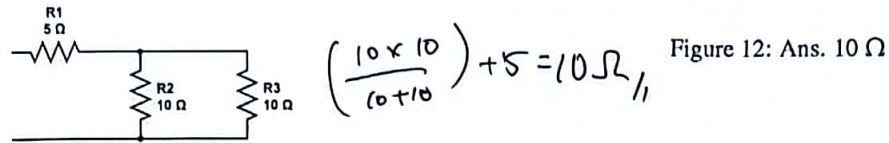


Figure 12: Ans. 10 Ω

- (c) Find equivalent resistance of the circuit given in Fig.13.

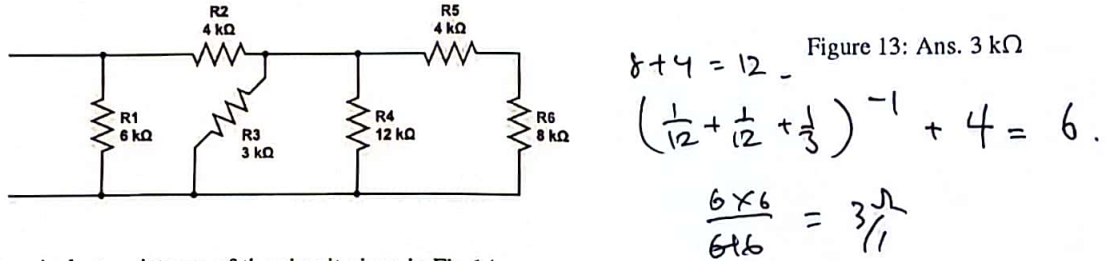


Figure 13: Ans. 3 kΩ

- (d) Find equivalent resistance of the circuit given in Fig.14.

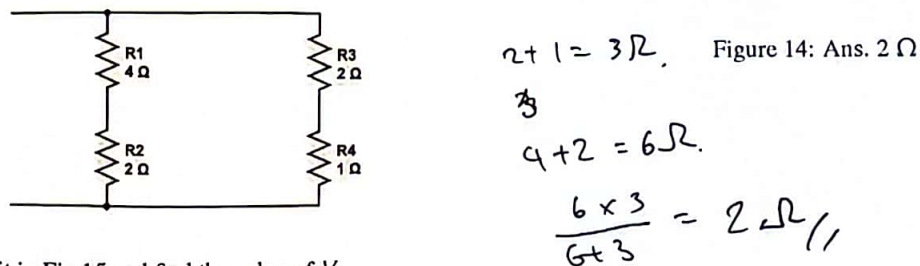


Figure 14: Ans. 2 Ω

- (e) Solve the circuit in Fig.15 and find the value of V.

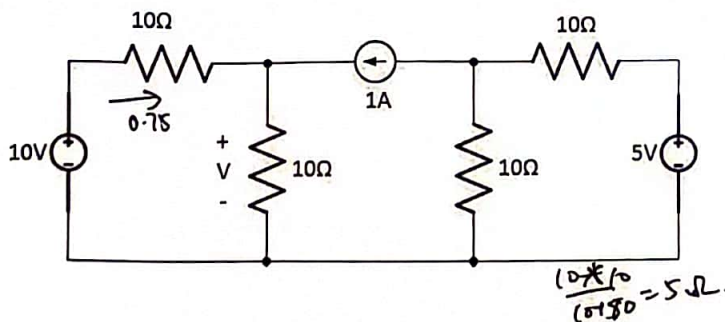


Figure 15: Additional practice problem

$$\left(\frac{1}{10} + \frac{1}{10} + \frac{1}{10}\right)^{-1} = \frac{10}{3}$$

$$10 + \frac{10}{3} = \frac{40}{3}\Omega$$

$$I_{V1} = \frac{10}{40/3} = 0.75A$$

$$\frac{5}{5 + 10} \times 0.75 = 0.25A$$


$$I_{V2} = \frac{5}{40/3} = \frac{3}{8}A$$

$$\frac{10}{10 + 5} \times \frac{3}{8} = 0.25$$

$$V = 1 \times 10 = 10V //$$

$$\frac{10}{10 + 10} \times 1 = 0.5A$$

$$I_V = 0.5 + 0.25 + 0.25 = 1A$$

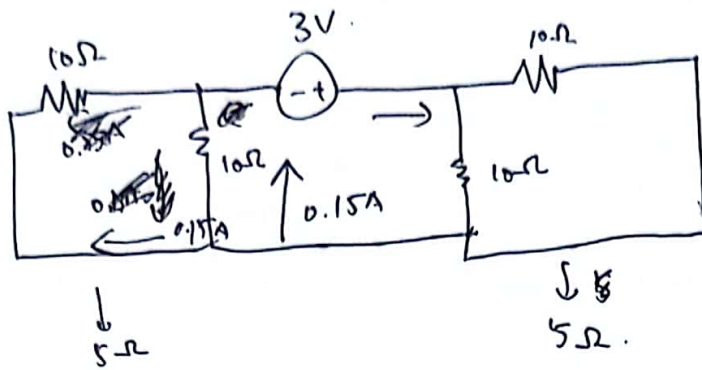

V
 I

$$R_T = 5 + 5 = 10 \Omega$$

$$V_R I_{R_T} = \frac{3}{10} \text{ A}$$

$$\frac{10}{10+10} \times \frac{3}{10} = \frac{3}{20} \approx \underline{0.15 \text{ A}}$$


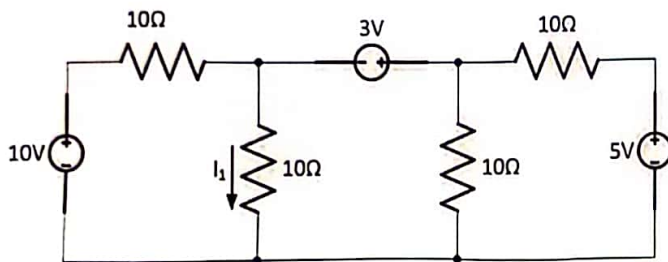


Figure 16: Additional practice problem

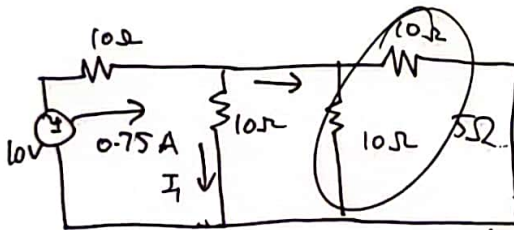

$$\left(\frac{1}{10} + \frac{1}{10} + \frac{1}{10} \right)^{-1} = \frac{10}{3}$$

$$\frac{10 \times 10}{10+10} = 5$$

$$R_T = \frac{10}{3} + 10 = \frac{40}{3} \Omega$$

$$I_{R_T} = \frac{10}{40/3} = 0.75 \text{ A}$$

$$I_1 = \frac{5}{10+5} \times 0.75$$

$$= \underline{0.25 \text{ A}}$$



$$I_{R_T} = \frac{5}{40/3} = \frac{3}{8}$$

$$\frac{10}{10+5} \times \frac{3}{8} = \frac{1}{4}$$

$$\frac{1}{4} \times \frac{10}{10+10} = \frac{1}{8} \text{ A} \Rightarrow \underline{0.125 \text{ A}}$$

$$\cancel{0.25 + 0.125 - 0.15 =}$$

$$\therefore 0.25 + 0.125 - 0.15 = 0.225 \text{ A}$$