

# Chapter 27 Direct-Current Circuits

## Conservation Principles

- **Conservation of Charges:** At any junction in a circuit, the total current entering must equal the total current leaving.
- **Conservation of Energy:** For any closed loop in a circuit, the sum of changes in potential energy must be zero.

## Definition of Direct Current


- **Direct Current (DC):** A type of electrical current that maintains a constant magnitude and direction.
- Batteries generate DC because the potential difference between their terminals remains steady.
- The electromotive force (emf), denoted as  $\epsilon$ , represents the maximum voltage a battery can supply between its terminals.

## Key Points on E.M.F.

- **E.M.F. is not a force** but a measure of energy provided per unit charge by a source.
- The voltage across an open circuit equals the emf.
- Terminal voltage  $\Delta V$  can be expressed as:

$$\Delta V = \epsilon - Ir$$

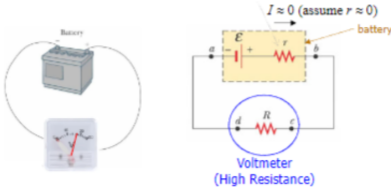where  $r$  is the internal resistance of the battery and  $I$  is the current.




## Resistors in Series

- Resistors are in series if connected end-to-end, and the same current flows through each resistor.
- The total or equivalent resistance for series resistors:

$$R_{\text{eq}} = R_1 + R_2 + R_3 + \dots$$

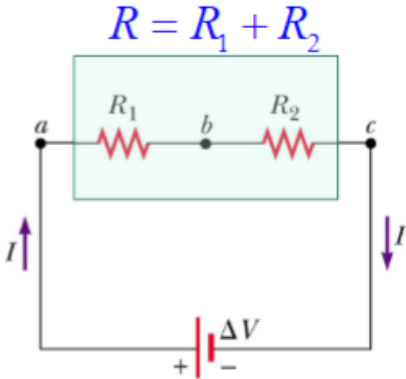- The voltage divides across the series components proportionally.




## Resistors in Parallel

- Each parallel resistor shares the same potential difference but divides the total current.
- Equivalent resistance for parallel resistors:

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

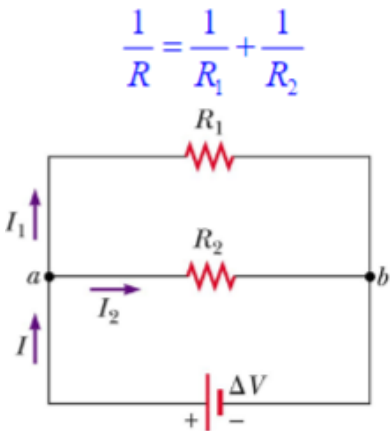- The equivalent resistance is always less than the smallest individual resistance.



## Kirchhoff's Rules

### Junction Rule


- States that the sum of currents at any junction is zero:

$$\sum I_{\text{in}} = \sum I_{\text{out}}$$

### Loop Rule

- States that the sum of the potential differences around any closed loop must be zero:

$$\sum \Delta V_{\text{loop}} = 0$$

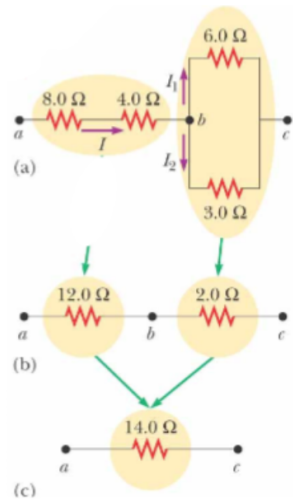

Problem-Solving Strategy

- Diagram:** Sketch the circuit and label all known and unknown values.
- Direction of Current:** Assign current directions arbitrarily but remain consistent.
- Apply Rules:** Use the junction rule for current and the loop rule for potential differences as needed.
- Solve Equations:** Simultaneously solve the equations for unknown quantities.
  - A negative current result means the current flows in the opposite direction to what was assigned.

**Example.** Calculate the current flow in each resistor shown in figure.

**Answer:**

Let the currents be as shown.

We apply Kirchhoff's rules to the diagram.

$50 - 2I_1 - 2I_2 = 0 \dots (1)$  $20 - 2I_3 + 2I_2 = 0 \dots (2)$  $I_1 = I_2 + I_3 \dots (3)$

Sub (3) to (1)  $\rightarrow 50 - 2(I_2 + I_3) - 2I_2 = 0$   
 $\rightarrow 50 - 4I_2 - 2I_3 = 0 \rightarrow -2I_3 = 4I_2 - 50 \dots (4)$

Sub (4) to (2)  $\rightarrow 20 + (4I_2 - 50) + 2I_2 = 0 \rightarrow 6I_2 - 30 = 0 \rightarrow I_2 = \boxed{5 \text{ A}}$

(1)  $\rightarrow 2I_1 = 50 - 2I_2 = 50 - 2(5) = 40 \text{ A} \rightarrow I_1 = \boxed{20 \text{ A}}$

(3)  $\rightarrow I_3 = I_1 - I_2 = 20 - 5 = \boxed{15 \text{ A}}$

*Traditional approach presented in Textbook!!*

*These are algebraic all.*

$R = \frac{\Delta V}{I} \rightarrow \Delta V = IR$

**Simplified Approach I**  
have learnt from MIT  
Professor Walter Lewin  
from YouTube video:

Let the **partial** current in each cycle be as shown.

We apply Kirchhoff's rules to the diagram.

$50 - 2I_1 + 2(-I_1 + I_2) = 0$  $\rightarrow 50 - 4I_1 + 2I_2 = 0 \dots (1)$  $20 - 2I_2 + 2(-I_2 + I_1) = 0$  $\rightarrow 20 - 4I_2 + 2I_1 = 0 \dots (2)$

(2) x 2:  $40 - 8I_2 + 4I_1 = 0 \dots (3)$

(1) + (3):  $90 - 6I_2 = 0 \rightarrow I_2 = \boxed{15 \text{ A}}$

(2):  $20 - 4 \times 15 + 2I_1 = 0 \rightarrow I_1 = \boxed{20 \text{ A}}$

*Simplified approach*

*These are algebraic all.*

$R = \frac{\Delta V}{I} \rightarrow \Delta V = IR$

Power Distribution

- Total power output of a battery:

$$P = I\epsilon$$

- Power delivered to an external resistor:

$$P = I^2R$$

To find the power delivered to each resistor, we apply  $P = I^2R$  to each resistor:

(2.00 Ω):  $P = (20 \text{ A})^2 (2 \text{ Ω}) = \boxed{800 \text{ W}}$

(4.00 Ω):  $P = (2.5 \text{ A})^2 (4.00 \text{ Ω}) = \boxed{25.0 \text{ W}}$

(2.00 Ω):  $P = (15.0 \text{ A})^2 (2.00 \text{ Ω}) = \boxed{450 \text{ W}}$

2 / 2